

## UNIT-6

# Sequential Logic Circuits Applications

## Counter:

Asynchronous and Synchronous

# What is Counter?

- A counter is a sequential circuit that goes through a prescribed sequence of states upon the application of input pulses.
- It is a cascade combination of multiple flip-flops to which the clock pulse is provided.
- Counters are generally used for the purpose of counting in digital circuits and the total number of counts represent the number of clock pulses arrived.

■ Two types of counters:

- ❖ synchronous (clocked /parallel) counters
- ❖ asynchronous (ripple) counters

■ Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.

■ Synchronous counters apply the same clock to all flip-flops.

# Difference between synchronous and asynchronous

Synchronous	Asynchronous
All flip flops in a synchronous counter are <b>triggered simultaneously</b> by the <b>same clock</b> .	Various flip-flops are activated with different clocks rather than simultaneously in an asynchronous counter.
<b>Operation speed</b> of a synchronous counter is faster as compared to that of an asynchronous counter.	The operation speed of an asynchronous counter is comparatively slower than a synchronous counter
There is <b>no propagation</b> delay observed in case of Synchronous Counters	There is a subsequent propagation delay from one flip-flop to another.
A Synchronous counter can be operated in <b>any desired count sequence</b> , as it could get manipulated by changing the clock sequence.	An Asynchronous counter can operate only in a fixed count sequence, i.e., UP and DOWN
Examples of synchronized counters are Johnson and Ring counters.	Ripple UP counter and Ripple DOWN counter are two instances of asynchronous counters.



# MCQ

Asynchronous counters are known as



- (A) Ripple counters
- (B) Multiple clock counters
- (c) Decade counters
- (D) Modulus counter

# Asynchronous Counter


two-bit asynchronous binary counter

  

3-bit asynchronous counter

  
 
### 4-stage positive edge triggered ripple counter




$$\text{Frequency at output } Q_A = \frac{F_{CLK}}{2}$$

$$\text{Frequency at output } Q_B = \frac{Q_A}{2} = \frac{F_{CLK}}{4}$$


$$\text{Frequency at output } Q_C = \frac{Q_B}{2} = \frac{Q_A}{4} = \frac{F_{CLK}}{8}$$

$$\text{Frequency at output } Q_D = \frac{Q_C}{2} = \frac{Q_B}{4} = \frac{Q_A}{8} = \frac{F_{CLK}}{16}$$


### 4-bit asynchronous down counter

 
 
## Synchronous (clocked /parallel) counters




When negative edge of the first clock pulse is applied, flip-flop A will toggle because  $J_A = K_A = 1$ , whereas flip-flop B output will remain zero because  $J_B = K_B = 0$ . After first clock pulse  $Q_A = 1$  and  $Q_B = 0$ . At negative going edge of the second clock pulse both flip-flops will toggle because they both have a toggle condition on their J and K inputs ( $J_A = K_A = J_B = K_B = 1$ ). Thus after second clock pulse,  $Q_A = 0$  and  $Q_B = 1$ . At negative going edge of the third clock pulse flip-flop A toggles making  $Q_A = 1$ , but flip-flop B remains set i.e.  $Q_B = 1$ . Finally, at the leading edge of the fourth clock pulse both flip-flops toggle as their JK inputs are at logic 1. This results  $Q_A = Q_B = 0$  and counter recycled back to its original state. The timing details of

 


CP	$Q_B$	$Q_A$
0	0	0
1	0	1
2	1	0
3	1	1



## 3-bit Synchronous Binary Up Counter

 

CP	Q <sub>C</sub>	Q <sub>B</sub>	Q <sub>A</sub>
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

 

## Design Steps of 3 bit Synchronous counter

*Step 1: Find the number of flip flops.*

*Step 2: Choose the type of flip flop.*

*Step-3: Draw state diagram for the counter.*

*Step-4: Obtain excitation table for the counter.*

*Step 5: Derive the flip flop input functions (use K-Map)*

*Step-6: Draw the logic diagram of the counter.*



**For  $J_c$**

$Q_B Q_A$ $Q_C$		00	01	11	10
		0	0	1	0
	1	X	X	X	X

$$J_c = Q_B Q_A$$

**For  $K_c$**

$Q_B Q_A$ $Q_C$		00	01	11	10
0	X	X	X	X	X
1	0	0	0	1	0

$$K_c = Q_B Q_A$$

**For  $J_B$**

$Q_B Q_A$ $Q_C$		00	01	11	10
0	0	0	1	X	X
	1	0	1	X	X

$$J_B = Q_A$$

**For  $K_B$**

$Q_B Q_A$ $Q_C$		00	01	11	10
0	X	X	1	0	
1	X	X	1	0	

$$K_B = Q_A$$

**For  $J_A$**

$Q_B Q_A$ $Q_C$		00	01	11	10
0	1	X	X	1	
1	1	X	X	1	


$$J_A = 1$$

**For  $K_A$**

$Q_B Q_A$ $Q_C$		00	01	11	10
0	X	1	1	X	
1	X	1	1	X	

$$K_A = 1$$

# Decade Counter

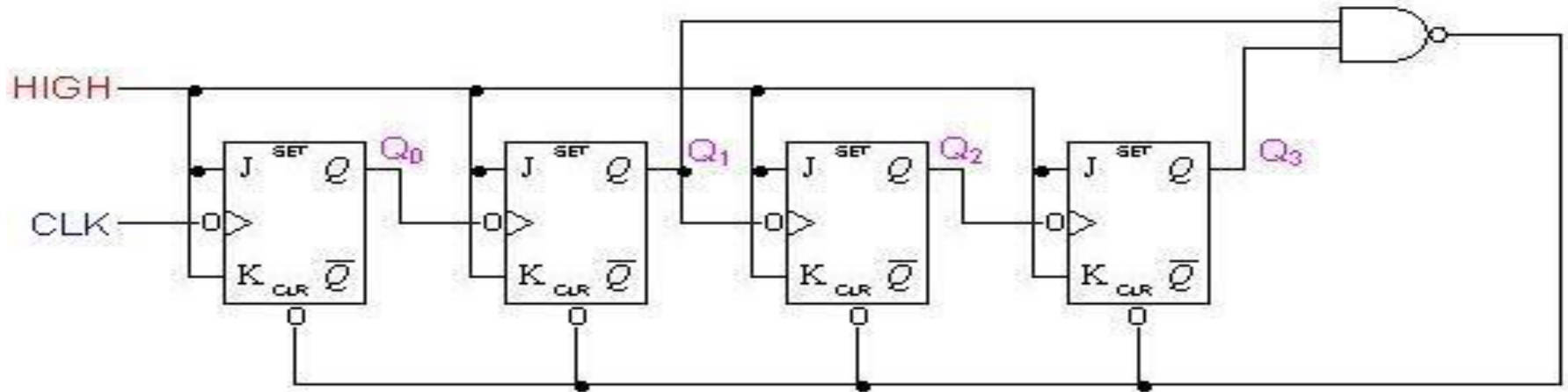

Once the counter counts to ten (1010), all the flip-flops are being cleared.

Clock Pulse	Q3	Q2	Q1	Q0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1