
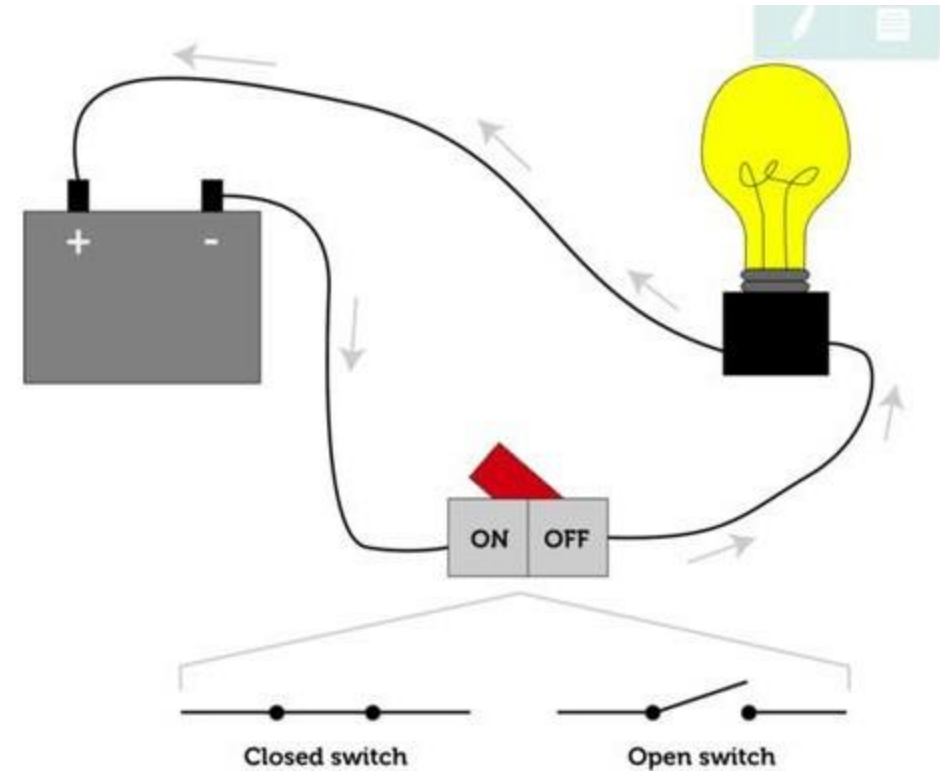


UNIT 1: DC CIRCUITS

Electrical Circuit

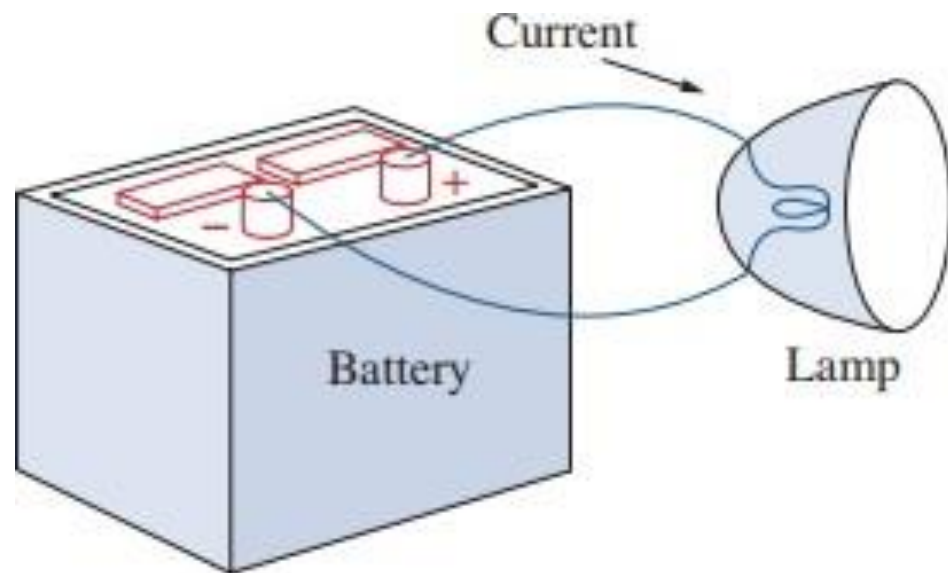

LOVELY
PROFESSIONAL
UNIVERSITY



Charge and Current

- **Charge:** Charge is an electrical property of the atomic particles of a matter.

S.I Unit: Coulomb (C)

Symbol: Q


- **Current:** Rate of change of charge.

OR

Continuous flow of electrons in an electrical circuit.

S.I Unit: Ampere (A)

Symbol: I

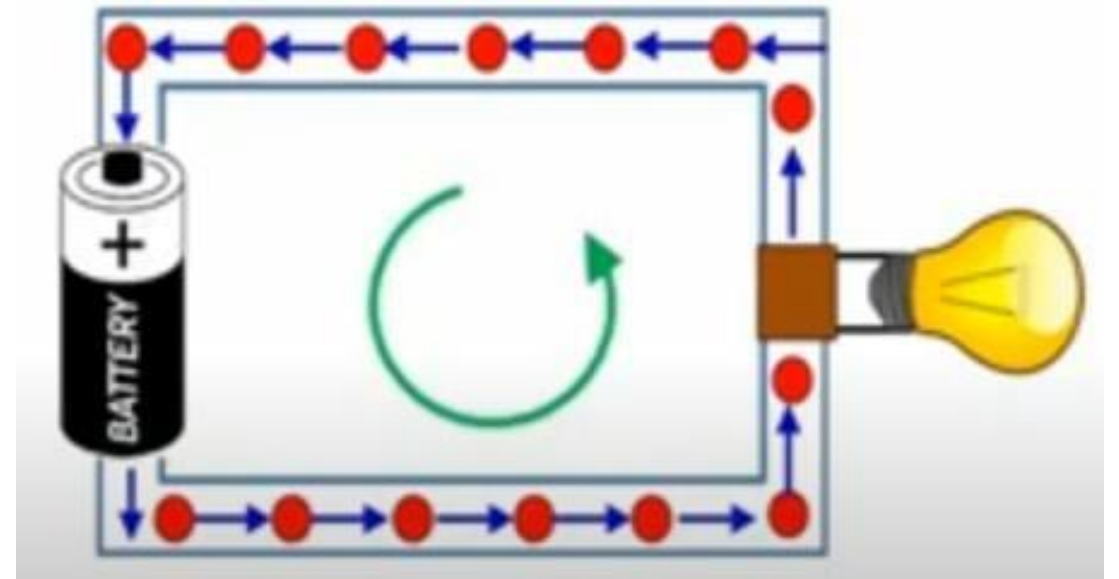

Charge and Current



LOVELY
PROFESSIONAL
UNIVERSITY

- Mathematically,

$$I = \frac{dQ}{dt} \text{ or } Q = \int_{t_0}^t I \cdot dt$$

Or, in simple terms:

$$I = \frac{Q}{T}$$

So, 1 Ampere = 1 coulomb/ 1 second.

QUICK QUIZ (Poll 1)



L OVELY
P ROFESSIONAL
U NIVERSITY

1 Coulomb is same as:

- A. Watt /sec
- B. Ampere/sec
- C. Joule-sec
- D. Ampere-sec

QUICK QUIZ (Poll 2)



L OVELY
P ROFESSIONAL
U NIVERSITY

The total charge entering the terminal is $5\sin 4\pi t \text{ mC}$. Calculate current at $t = 0.5 \text{ sec.}$:


- A. 31.2 A
- B. 31.2 mA
- C. 62.8 mA
- D. 62.8 A

Voltage

- It is the energy (Work) required to move a unit charge through an element.

S.I Unit: Volt (V)


Symbol: V

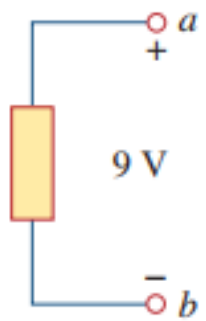

(a)

$$V_{ab} = -V_{ba}$$
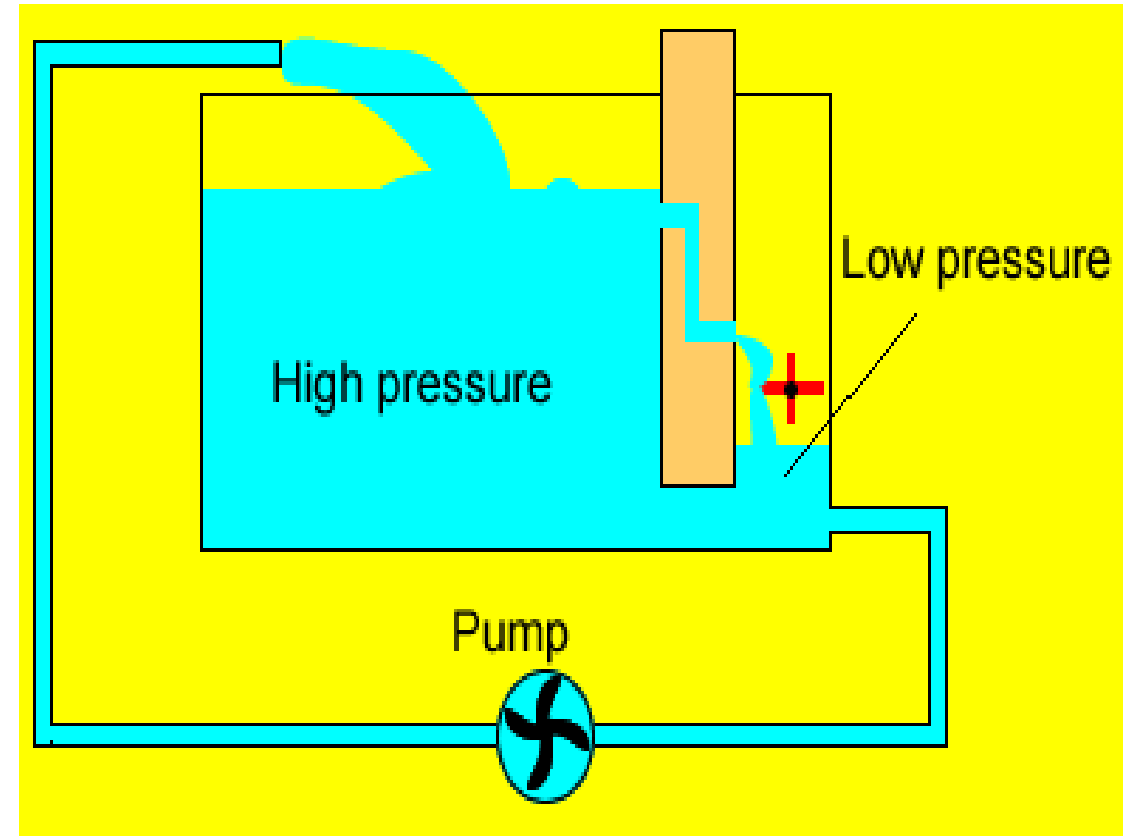
$$1 \text{ volt} = 1 \text{ joule/coulomb}$$



Power and Energy



LOVELY
PROFESSIONAL
UNIVERSITY

- **Power:** Rate at which the work is done.

OR

Time rate of absorbing or supplying energy

S.I Unit: Watts (W)

Symbol: P

Mathematically,

$$P = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt} = V \cdot I$$

Implies, $\boxed{P = V \cdot I}$

Power and Energy



L OVELY
P ROFESSIONAL
U NIVERSITY

- **Energy:** Capacity of doing work.
S.I Unit: Joules(J)
Symbol: E

QUICK QUIZ (Poll 3)



LOVELY
PROFESSIONAL
UNIVERSITY

Calculate the current ratings of 100 Watt incandescent bulb and 15 Watt LED lamp operated with the domestic supply of 220 Volt?

- A. Bulb = 0.068 A and LED = 0.45 A
- B. Bulb = 0.45 A and LED = 0.068 A
- C. Bulb = 0.50 A and LED = 0.068 A
- D. Bulb = 0.50 and LED = 0.68 A

QUICK QUIZ (Poll 4)



L OVELY
P ROFESSIONAL
U NIVERSITY

From the previous question, it can be inferred that:

- A. LED consumes 5 times more current than Bulb.
- B. Bulb consumes 5 times more current than LED..
- C. LED consumes 6.6 times more current than Bulb.
- D. Bulb consumes 6.6 times more current than LED.

Network Components



LOVELY
PROFESSIONAL
UNIVERSITY

Active


Battery

Transistor,
Op-amp,
Diode

VS and CS
Generators

Passive

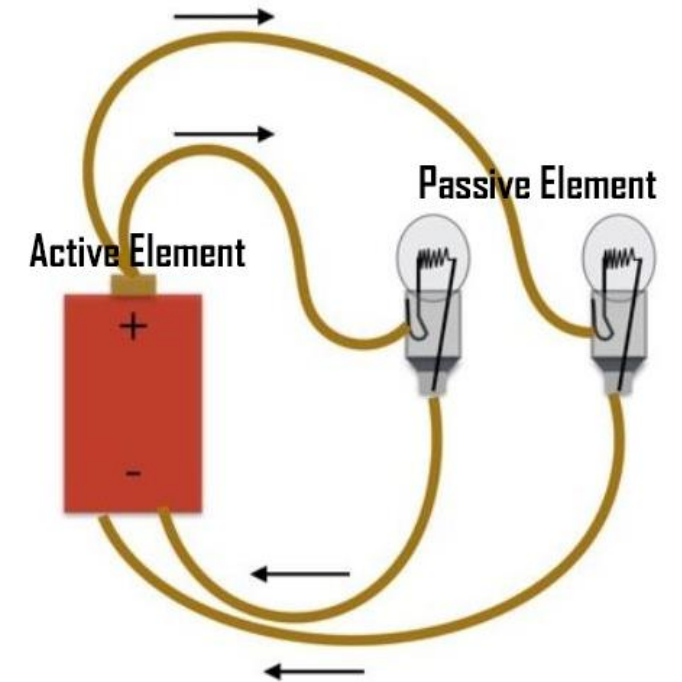Resistance (R)
Capacitance (C)
Inductance (L)
Transformers




Resistance

- **Resistance:** It is an opposition to the flow of current.

S.I Unit: Ohm (Ω)

Symbol: R

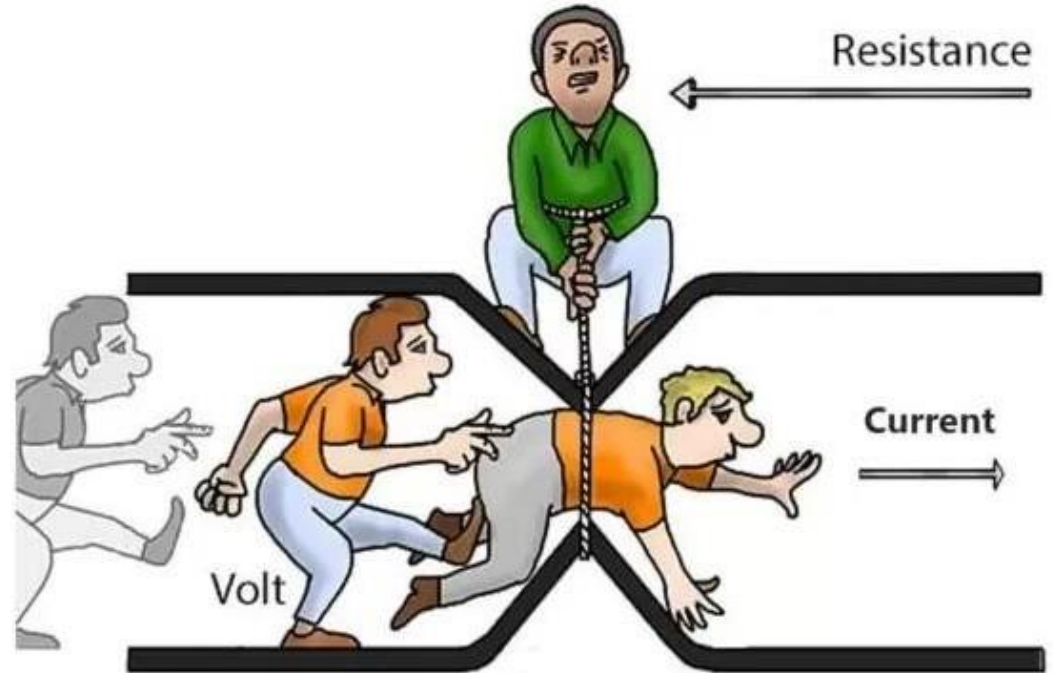

Capacitance


- **Capacitance** is the ability of a device to store electrical energy in an electrostatic field.
- A **capacitor** is a device that stores energy in the form of an electrical field..
- A capacitor is made of two conductors separated by a dielectric.

S.I Unit: Farad (F)

Symbol: C

Two important Properties:

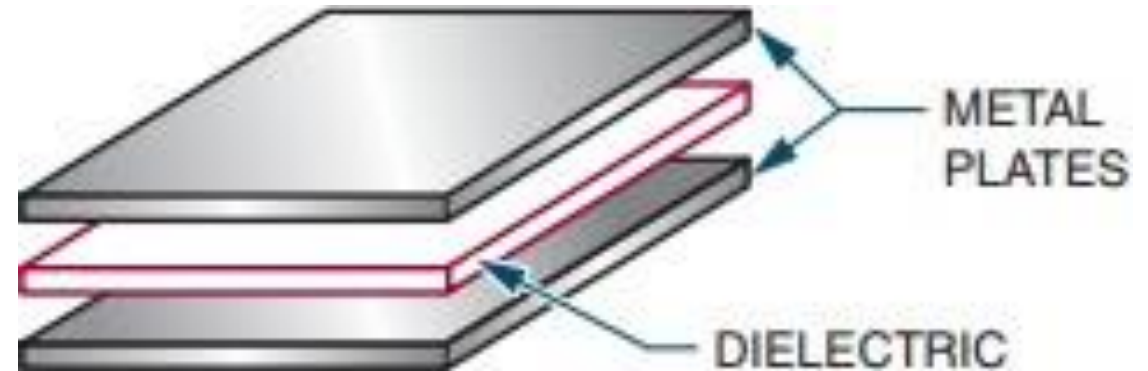1. No current flows through the capacitor, if the voltage remains constant.
2. Voltage across a capacitor cannot change instantaneously.



Inductance


- **Inductance** is the characteristic of an electrical conductor that opposes a change in current flow.
- An **inductor** is a device that stores energy in a magnetic field.
- When a current flows through a conductor, magnetic field builds up around the conductor. This field contains energy and is the foundation for inductance

S.I Unit: Henry (H)

Symbol: L

Two important Properties:

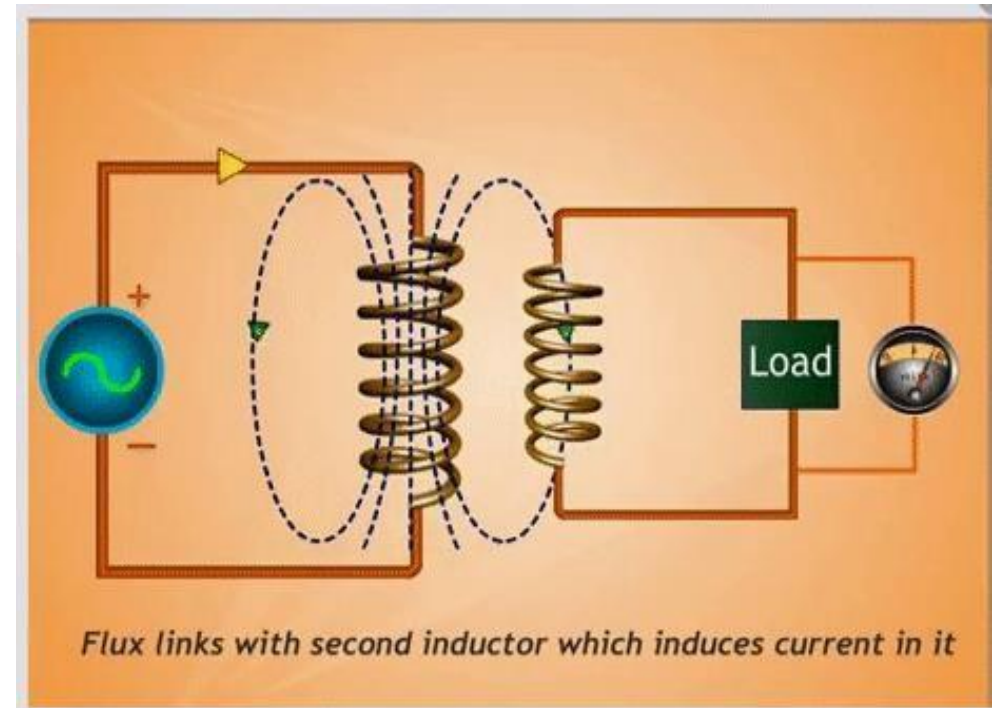1. No voltage appears across an inductor, if the current through it remains constant.
2. The current through an inductor cannot change instantaneously.




Capacitance and Inductance

- $Q = CV$

- $I = \frac{dQ}{dt} = \frac{d CV}{dt} = C \frac{dV}{dt}$

- $E = \frac{1}{2} CV^2$


- $C = \frac{A\epsilon}{d}$

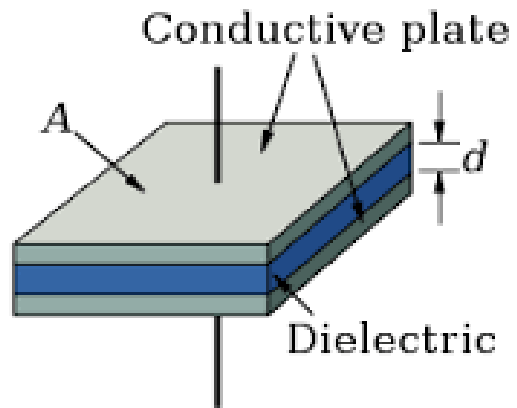

- $V = L \frac{dI}{dt}$

- $E = \frac{1}{2} LI^2$

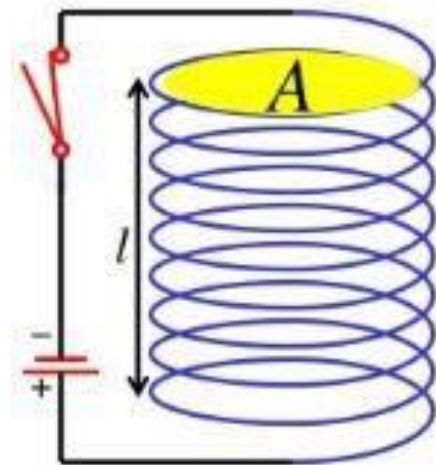- $L = \frac{\mu N^2 A}{l(\text{length of coil})}$



QUICK QUIZ (Poll 5)



L OVELY
P ROFESSIONAL
U NIVERSITY

Identify the passive element

- A. Battery
- ☒ B. Transformer
- C. Transistor
- D. OP-amp

QUICK QUIZ (Poll 6)



LOVELY
PROFESSIONAL
UNIVERSITY

Find the value of capacitance if the value of voltage increases linearly from 0 to 100 V in 0.1 s causing a current flow of 5 mA?

- A. 10 μF
- B. 5 F
- C. 10 F
- D. 5 μF

Ohm's Law



LOVELY
PROFESSIONAL
UNIVERSITY

- Ohm's law states that:

“the current in an electric circuit is directly proportional to the voltage across its terminals, provided that the physical parameters like temperature, etc. remain constant”


Mathematically,

$$I \propto V$$

Or,

$$I = \frac{V}{R}$$

Where, Resistance $R = \rho \frac{l}{A}$

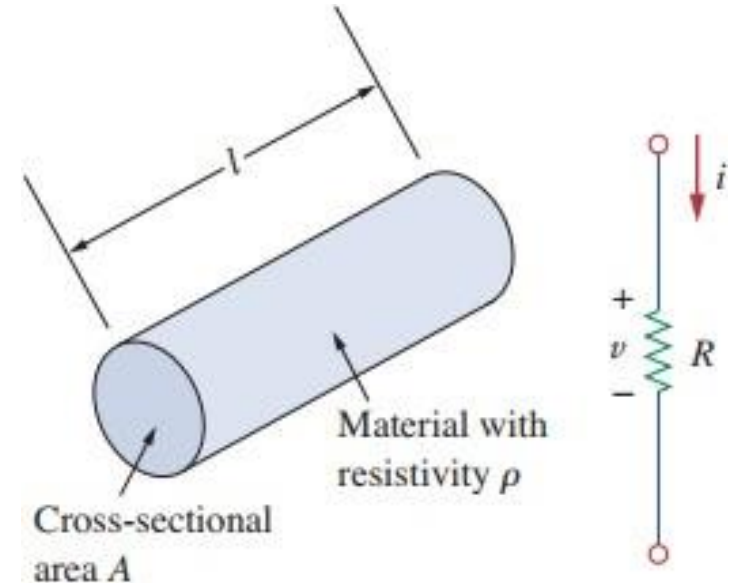

Resistivity Table



L OVELY
P ROFESSIONAL
U NIVERSITY

Material	Resistivity ($\Omega \cdot m$)	Usage
Silver	1.64×10^{-8}	Conductor
Copper	1.72×10^{-8}	Conductor
Aluminum	2.8×10^{-8}	Conductor
Gold	2.45×10^{-8}	Conductor
Carbon	4×10^{-5}	Semiconductor
Germanium	47×10^{-2}	Semiconductor
Silicon	6.4×10^2	Semiconductor
Paper	10^{10}	Insulator
Mica	5×10^{11}	Insulator
Glass	10^{12}	Insulator
Teflon	3×10^{12}	Insulator

Conductance



LOVELY
PROFESSIONAL
UNIVERSITY



- A useful quantity in circuit analysis is the **reciprocal** of resistance R , known as **conductance** and denoted by G
- $G = \frac{1}{R} = \frac{I}{V}$
- S.I Unit: mho (ohm spelled backwards) or Siemens
- Symbol: \mathcal{U} , the inverted omega.

$$1 \text{ S} = 1 \mathcal{U} = 1 \text{ A/V}$$



- Power dissipated in the resistor can be expressed as:


- $P = VI = I^2R = \frac{V^2}{R}$

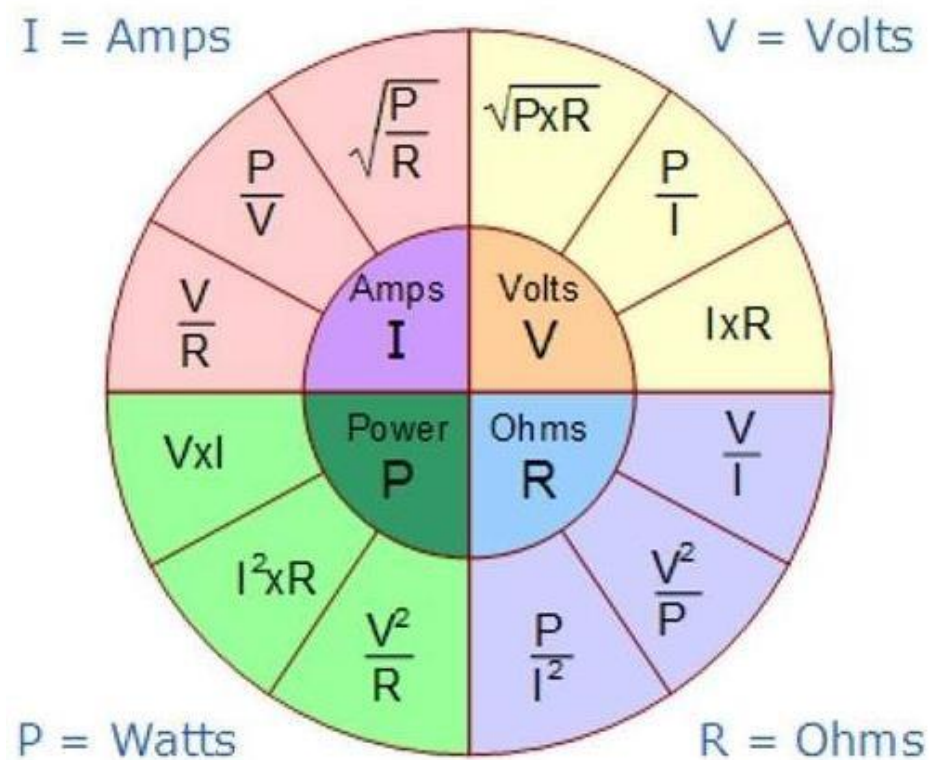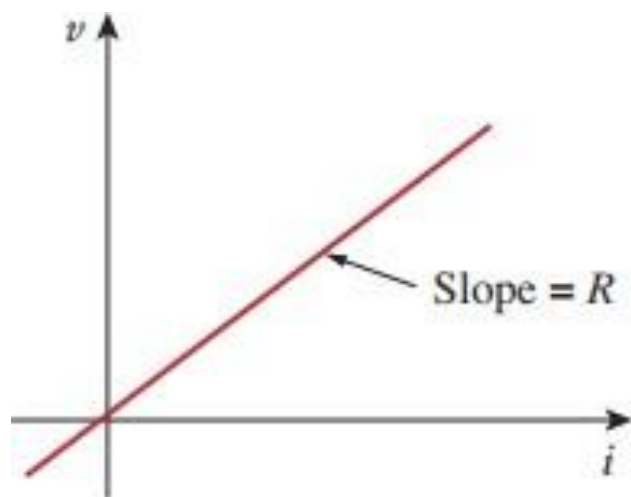


Ohm's Law Pie Chart (Source: Electronics-Tutorials.ws)

Short-circuit and Open-circuit

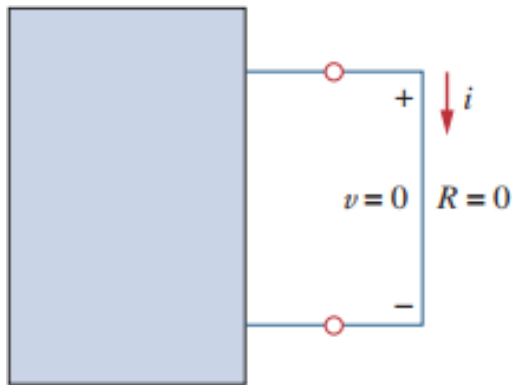- For a short circuit, $R = 0 \Omega$
- Therefore, $V = I.R = 0 \text{ V}$
- **NOTE:** (current, I can be of any value)



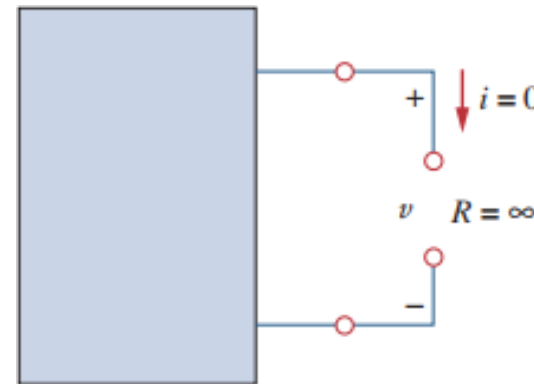- For an open circuit, $R = \infty \Omega$
- Therefore, $I = V/R = 0 \text{ A}$
- **NOTE:** (voltage, V can be of any value)



Applications of Ohm's Law



L OVELY
P ROFESSIONAL
U NIVERSITY

1. To find unknown Voltage (V)
2. To Find unknown Resistance (R)
3. To Find unknown Current (I)
4. Can be used to find Unknown Conductance (G)=1/R
5. Can be used to find unknown Power (P)=VI
6. Can be used to find unknown conductivity or Resistivity

$$v = iR$$

$$R = \frac{v}{i}$$

$$I = V/R$$

$$R = \rho \frac{\ell}{A}$$

Applications of Ohm's Law



LOVELY
PROFESSIONAL
UNIVERSITY


1. It is widely used in circuit analysis.
2. It is used in **ammeter, multimeter**, etc.
3. It is used to design resistors.
4. It is used to get the desired circuit drop in circuit design (Example, **Domestic Fan Regulator**).
5. Advanced laws such as Kirchhoff's law, Norton's law, Thevenin's law are based on ohm's law.
6. **Electric heaters, kettles** and other types of equipment working principle follow ohm's law.
7. **A laptop and mobile charger** using DC power supply in operation and working principle of DC power supply depend on ohm's law.

Limitations of Ohm's Law



LOVELY
PROFESSIONAL
UNIVERSITY

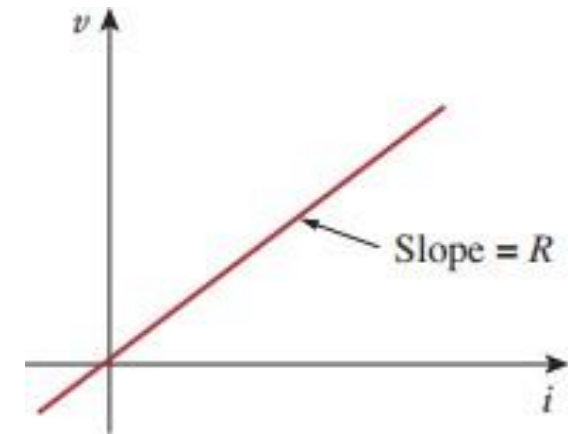- Ohm's law holds true only for a conductor at a **constant temperature**. Resistivity changes with temperature.
- Ohm's law by itself is not sufficient to analyze circuits.
- It is NOT applicable to **non linear elements**, For example, Diodes, Transistors, Thyristors, etc.
- This law cannot be applied to **unilateral networks**.




QUICK QUIZ (Poll 7)



LOVELY
PROFESSIONAL
UNIVERSITY

The voltage and the conductance of the given circuit is:

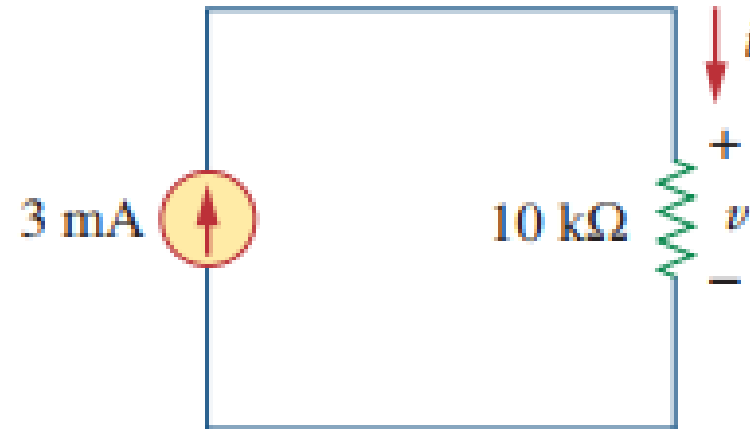- A. 30 V, $10\ \mu\text{S}$
- B. 30 mV, $100\ \mu\text{S}$
- C. 30 V, $100\ \mu\text{S}$
- D. 30 mV, $10\ \mu\text{S}$




QUICK QUIZ (Poll 8)



LOVELY
PROFESSIONAL
UNIVERSITY

The power of the given circuit is:

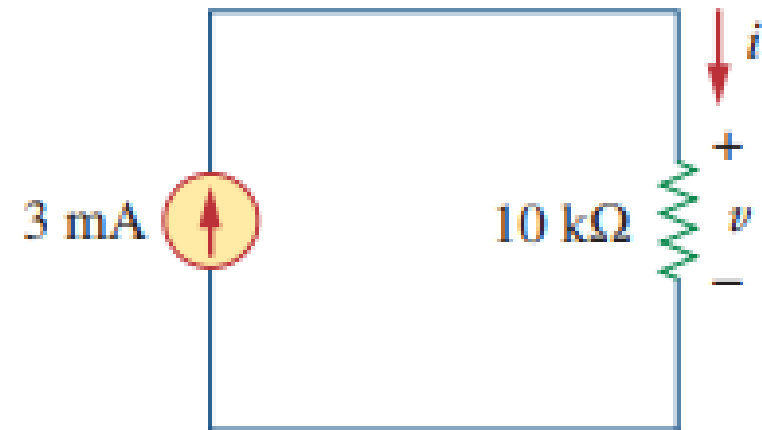- A. 60 mW
- B. 70 mW
- C. 80 mW
- D. 90 mW





Series Connection



LOVELY
PROFESSIONAL
UNIVERSITY

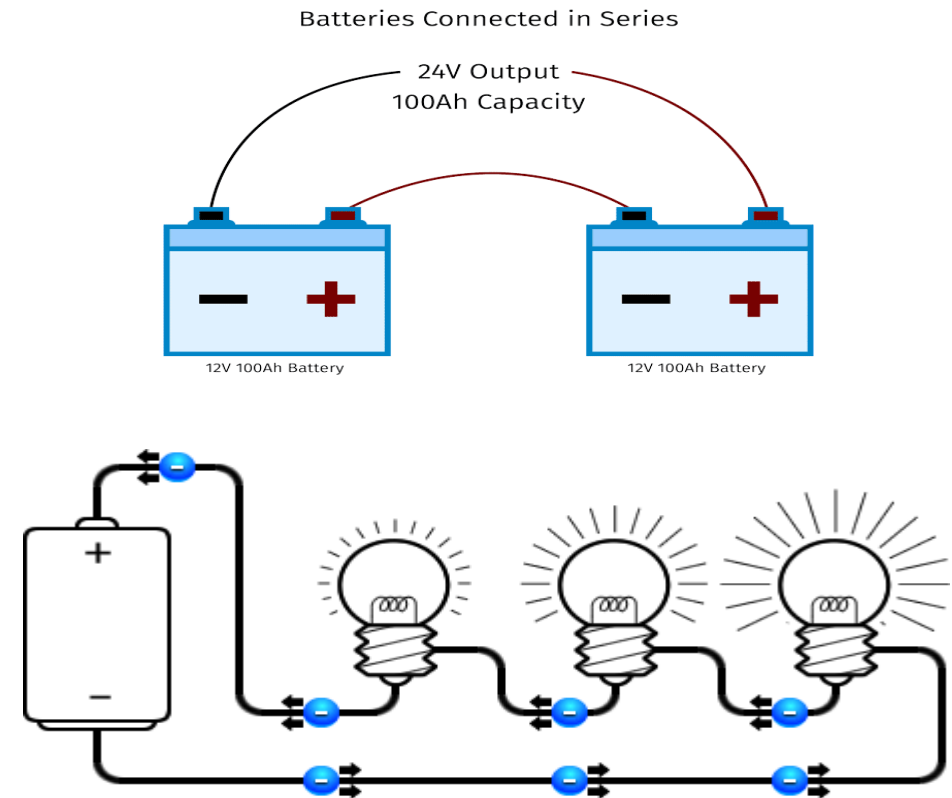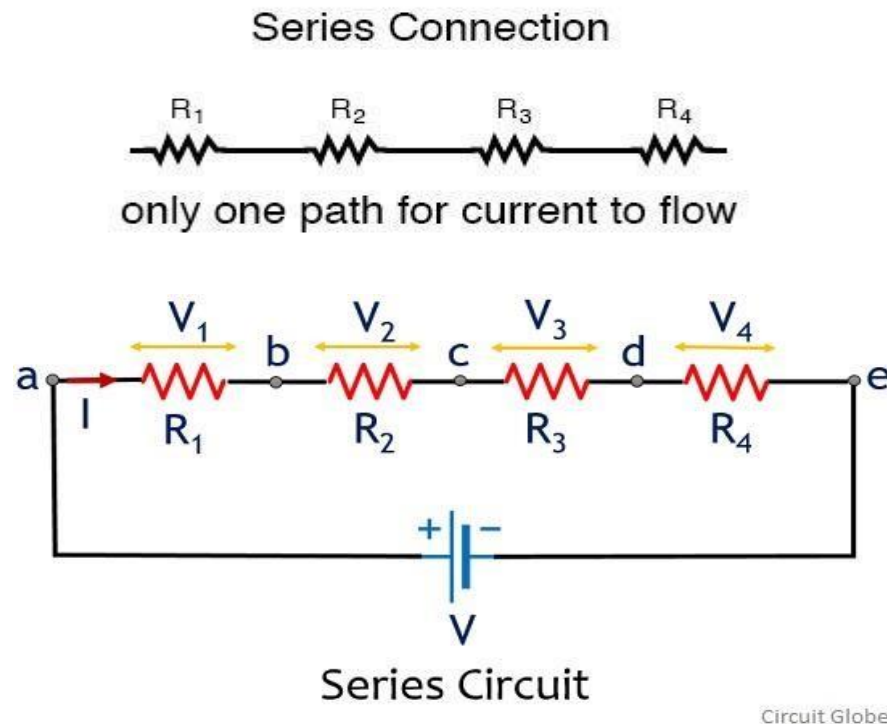- **SERIES CONNECTION:** Two or more elements are in series if they exclusively share a single node and consequently carry the same current.






In Series System Voltage are Added & Current are Same

Parallel Connection



LOVELY
PROFESSIONAL
UNIVERSITY

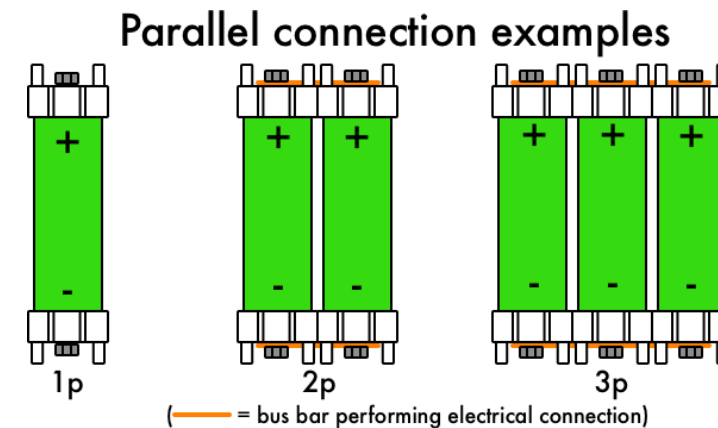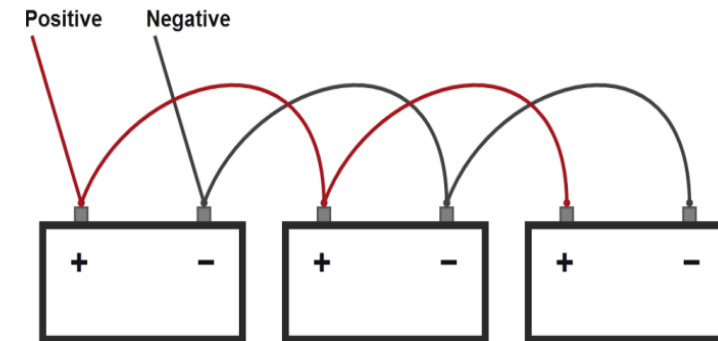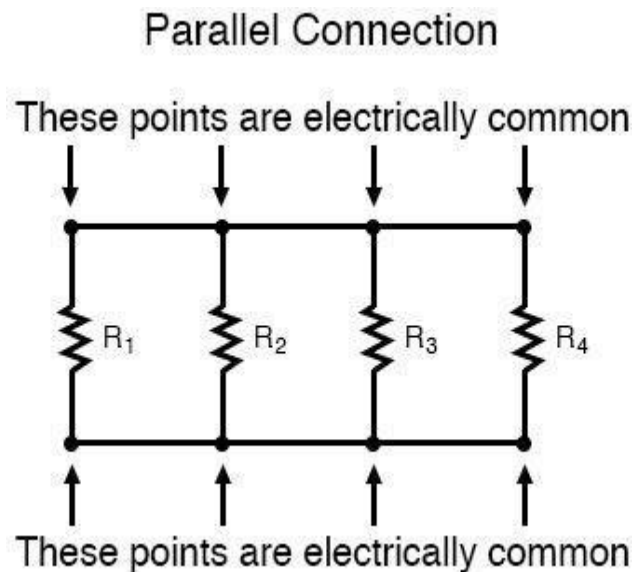- **PARALLEL CONNECTION:** Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them




Battery Voltage In Series And Parallel




LOVELY
PROFESSIONAL
UNIVERSITY


Series Circuit

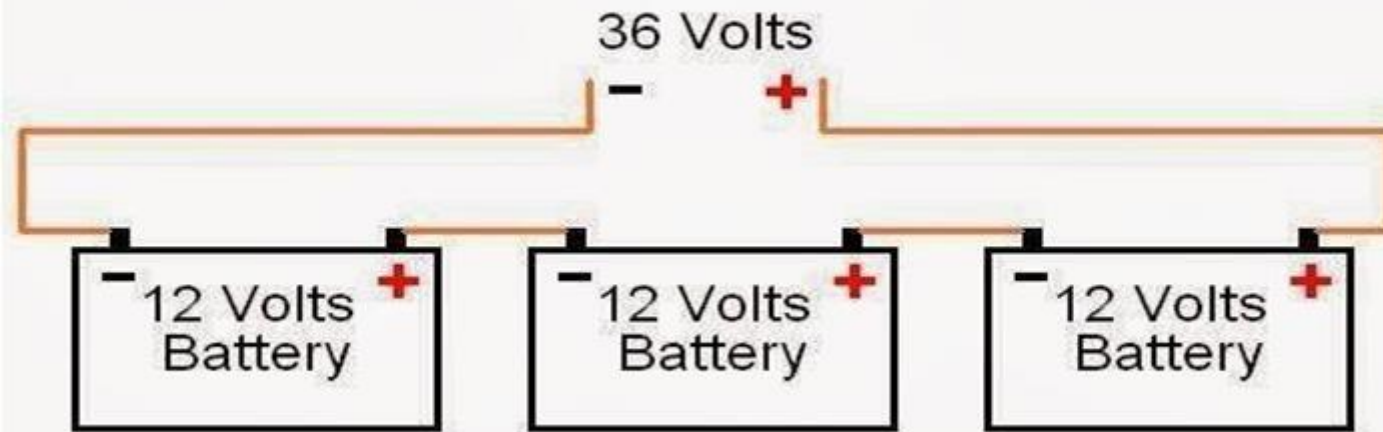


Batteries Joined in a Series

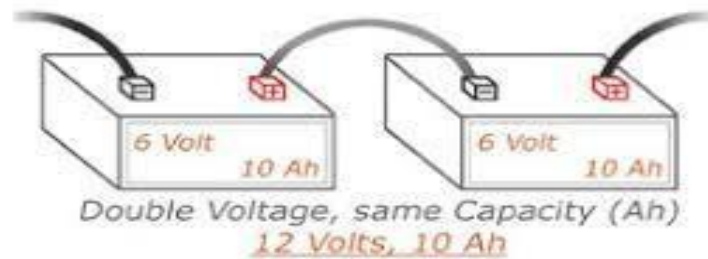

Parallel Circuit

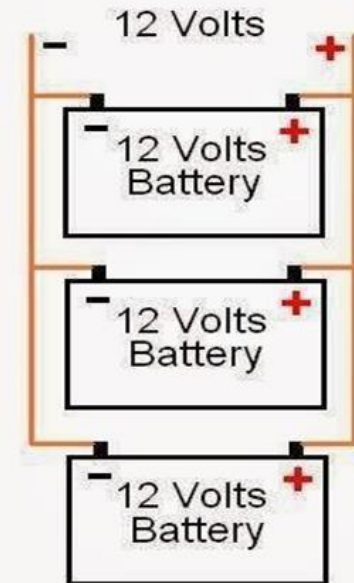


Supply Voltage
220V or 110V AC

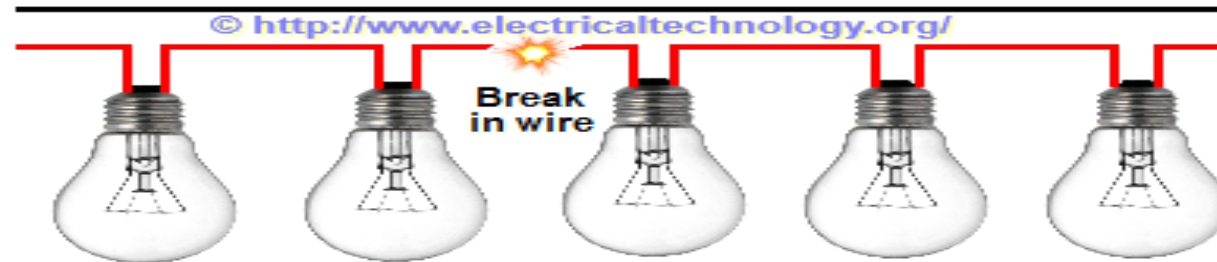

Series Connection

Supply Voltage
220V or 110V AC

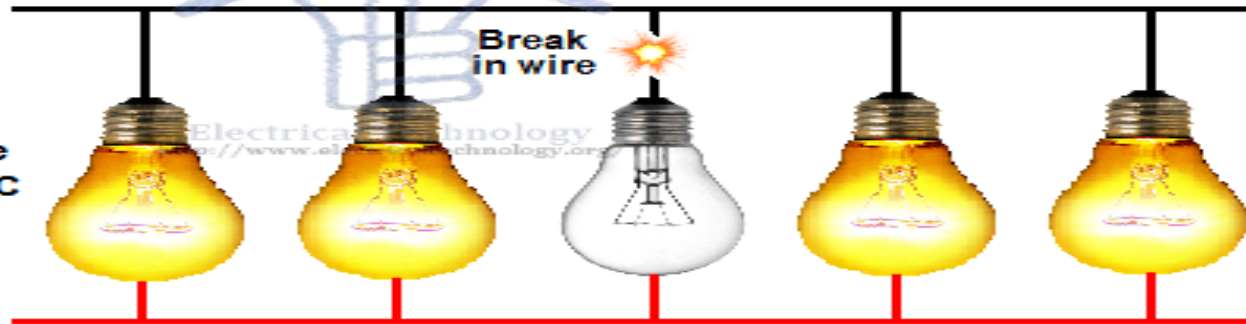

The rest of bulbs are ON

Parallel Connection

**Why Parallel Connection is
Preferred over Series Connection?**



LOVELY
PROFESSIONAL
UNIVERSITY

RESISTORS IN SERIES



Series: Two or more elements are in series if they are cascaded or connected sequentially and consequently carry the same current.



LOVELY
PROFESSIONAL
UNIVERSITY

The equivalent resistance of any number of resistors connected in a series is the sum of the individual resistances
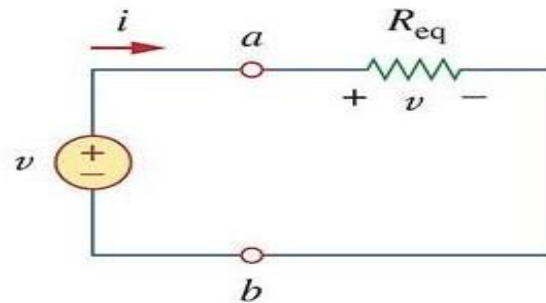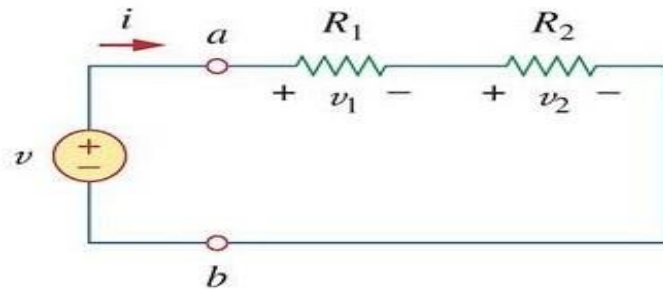
$$R_{eq} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$




Note: Resistors in series behave as a single resistor whose resistance is equal to the sum of the resistances of the individual resistors.

Resistors in Parallel



LOVELY
PROFESSIONAL
UNIVERSITY

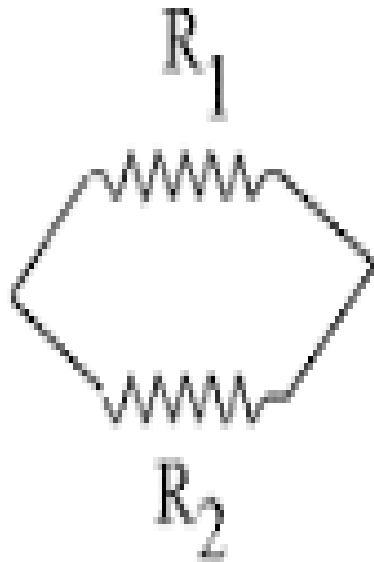

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_t} = \frac{R_2 + R_1}{R_1 R_2}$$

$$R_t = \frac{R_1 R_2}{R_2 + R_1}$$


The equivalent of two parallel resistor is equal to their product divided by their sum .

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

How to find Equivalent Resistance for Series-Parallel Combinations



LOVELY
PROFESSIONAL
UNIVERSITY

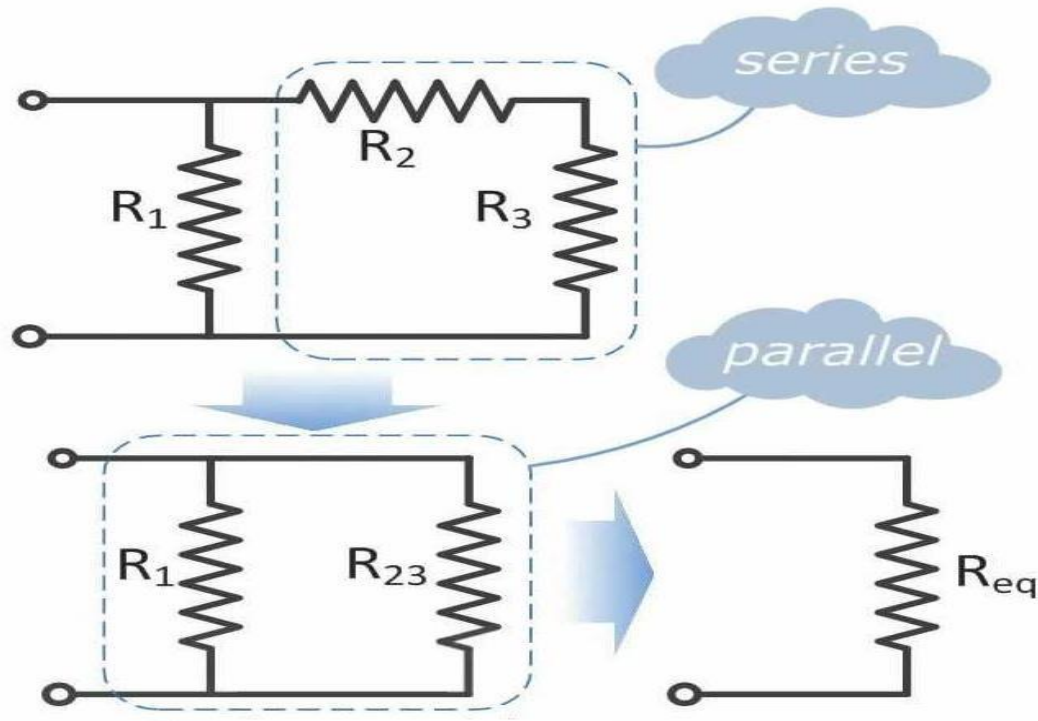

$$R_{23} = R_2 + R_3$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_{23}}$$

$$R_{eq} = \frac{R_1 \cdot R_{23}}{R_1 + R_{23}}$$



$$R_{eq} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

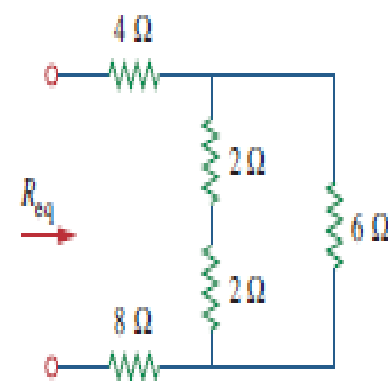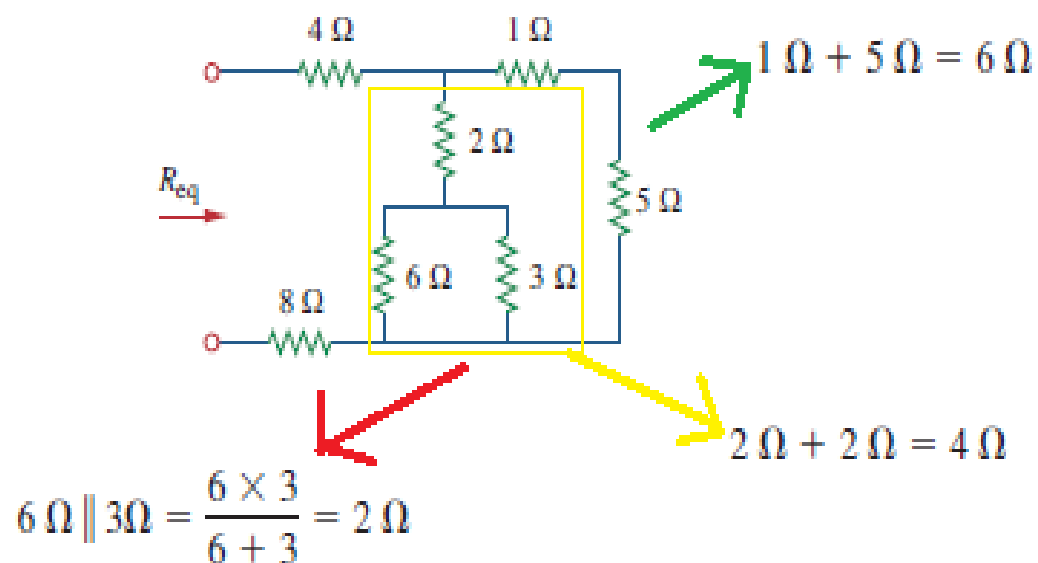Example: To find R_{eq}




LOVELY
PROFESSIONAL
UNIVERSITY

Find R_{eq} for the circuit shown in Fig.


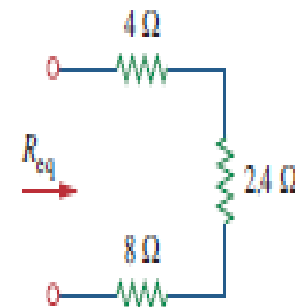
$$4\ \Omega \parallel 6\ \Omega = \frac{4 \times 6}{4 + 6} = 2.4\ \Omega$$



$$R_{eq} = 4\ \Omega + 2.4\ \Omega + 8\ \Omega = 14.4\ \Omega$$


QUICK QUIZ (Poll 9)



LOVELY
PROFESSIONAL
UNIVERSITY

Find Equivalent Resistance in Ohms?

- A. 5
- ☒ B. 10
- C. 15
- D. 20

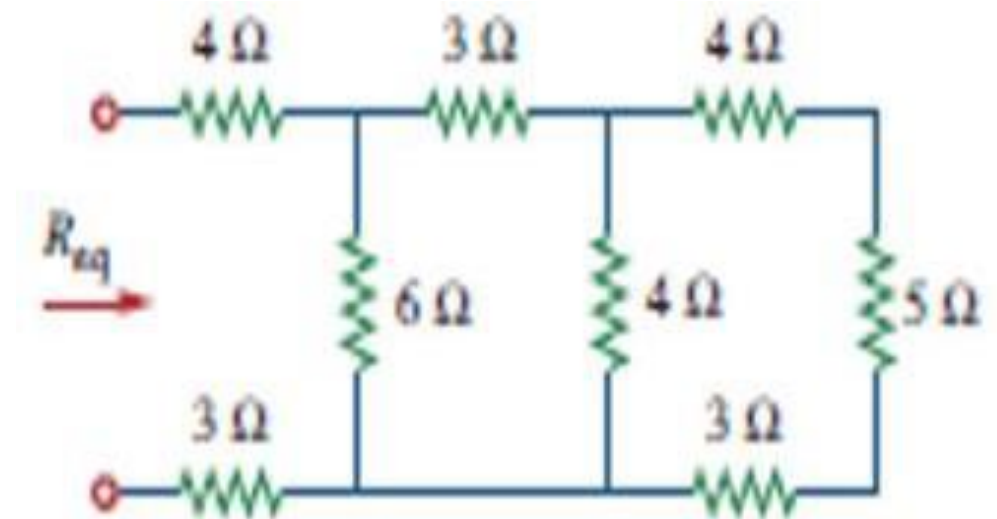

QUICK QUIZ (Poll 10)



LOVELY
PROFESSIONAL
UNIVERSITY

Find Equivalent Resistance in Ohms?

A. 12

B. 17

C. 19

D. 29

