

1. Find the equivalent resistance across terminal a-b as shown in Fig-1.

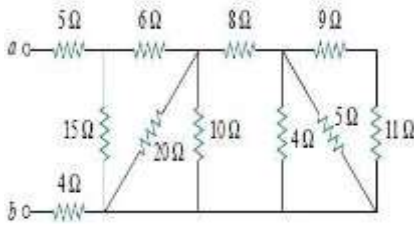


Fig-1

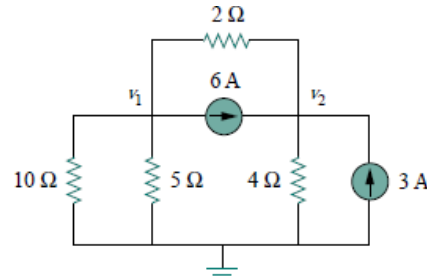


Fig-2

2. Obtain the node voltages in the circuit in Fig-2
3. Calculate the mesh currents i_1 and i_2 in the circuit of Fig-3.

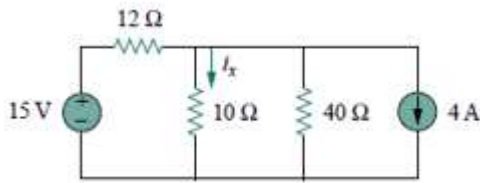


Fig.3

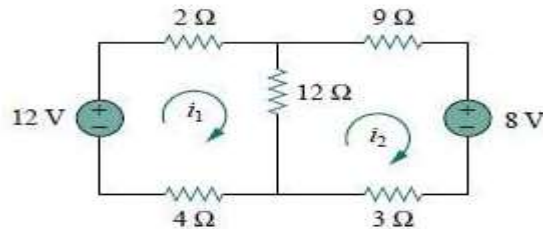


Fig.4

4. Calculate i_x and the power dissipated by the 10Ω resistor using superposition theorem as shown in Fig-4.
5. If voltage $v = 6 \cos(100t - 30^\circ)$ is applied to a 50 μF capacitor, calculate the current through the capacitor.
6. A current source in a linear circuit has is $i = 10 \cos(10^3 \pi t - 60^\circ)$ A.
(a) What is the amplitude of the current?
(b) What is the angular frequency?
(c) Find the frequency of the current.
(d) Calculate current at $t = 1$ ms

