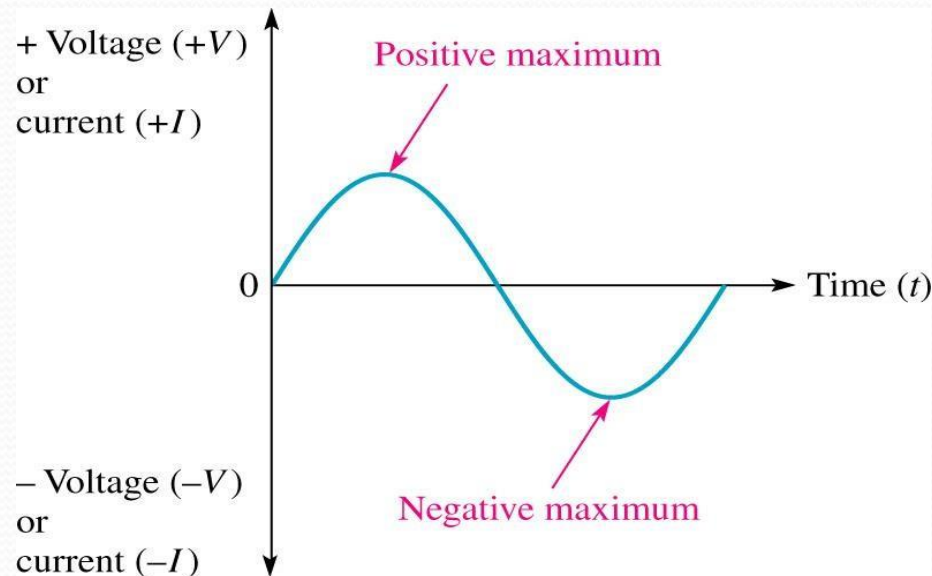


ECE-249

Unit-2

Fundamentals of A.C. circuits



Contents:



- Alternating Current
- Generating Ac Voltages
- Determination of Frequency (f) In The Ac Generator Fundamental
- Periodic Voltage Or Current Waveform
 - Average Value
 - Root Mean Square (RMS) Value
 - Average And RMS Values Of Sinusoidal Voltage Waveform
- Single-phase AC Supply
 - Purely Resistive Circuit (R Only)
 - Purely Inductive Circuit (L Only)
 - Purely Capacitive Circuit (C Only)

Cont:

- series A.C. circuit
 - R–L series A.C. circuit
 - R–C series A.C. circuit
 - R–L–C series A.C. circuit
- Three-phase AC Circuits
 - Generation of Three-phase Balanced Voltages
 - Delta(Δ)-Star(Y) conversion and Star-Delta conversion
 - Delta(Δ)-Star(Y) conversion and Star-Delta conversion impedance conduction


AC Fundamentals

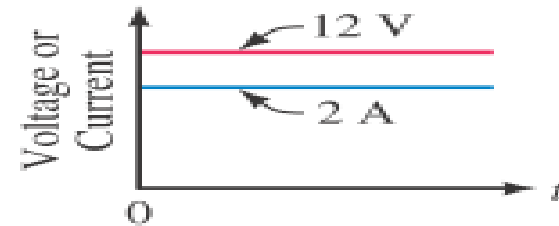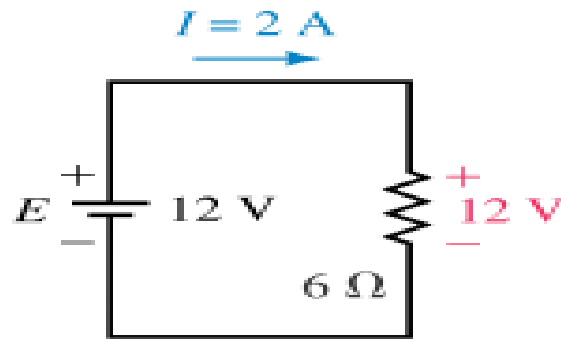- Previously you learned that **DC sources** have fixed polarities and constant magnitudes and thus produce currents with **constant value and unchanging direction**



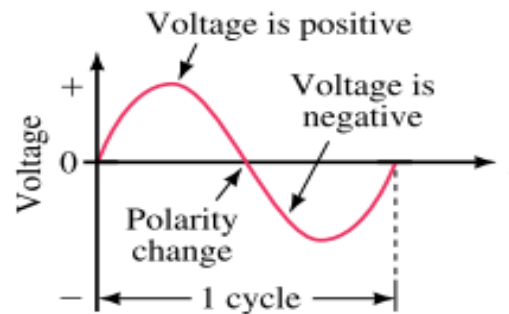
(b) Voltage and current versus time for dc

- In contrast, the **voltages of ac sources alternate** in polarity and vary in magnitude and thus produce currents that vary in magnitude and alternate in direction.




Generating AC Voltages

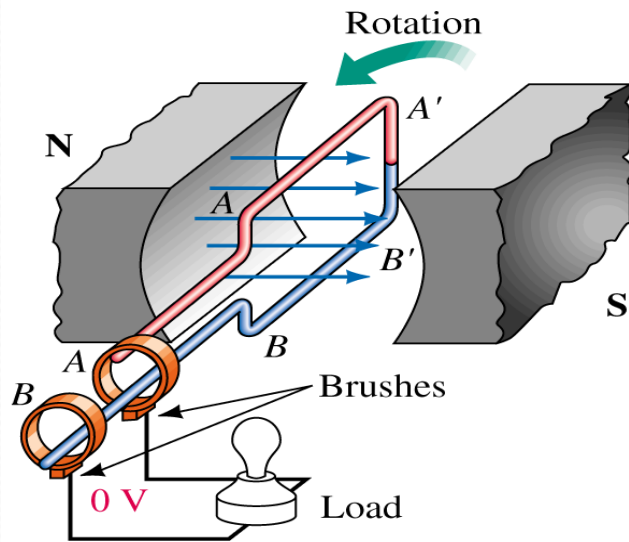- Generators convert rotational energy to electrical energy.
- Generate alternative emf by rotating a coil within a stationary magnetic field.
- Another way to rotating magnetic field a within a stationary coil.



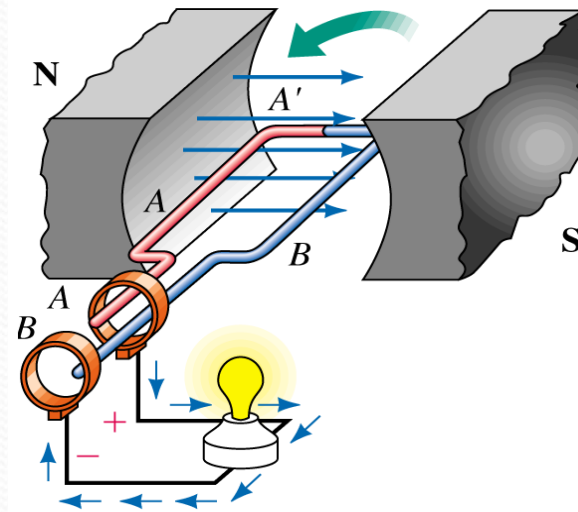
(a) 0° Position: Coil sides move parallel to flux lines. Since no flux is being cut, induced voltage is zero.



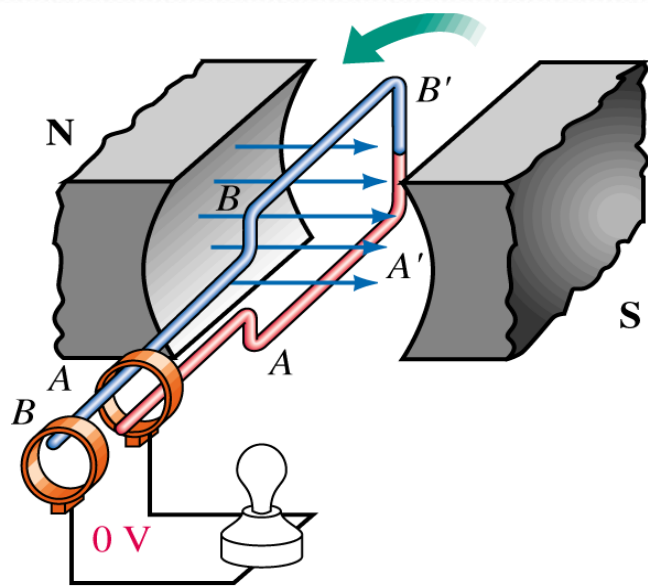
(b) 90° Position: Coil end A is positive with respect to B. Current direction is out of slip ring A.

Cont....

- The armature has an induced voltage, which is connected through slip rings and brushes to a load.
- The armature loops are wound on a magnetic core



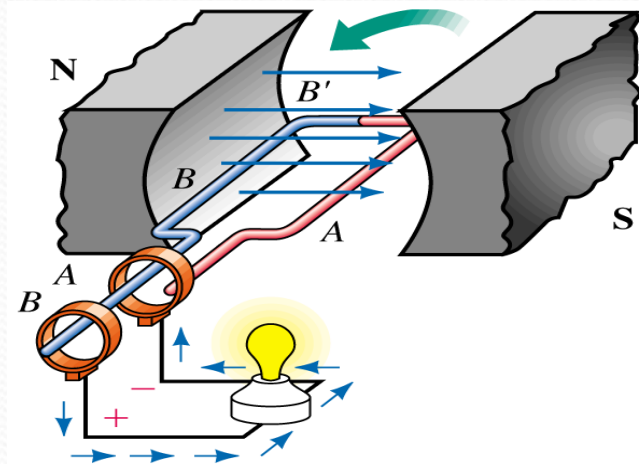(c) 180° Position: Coil again cutting no flux. Induced voltage is zero.




(d) 270° Position: Voltage polarity has reversed, therefore, current direction reverses.

- A multi-turn coil is placed inside a magnet with an air gap as shown in above Fig.
- The flux lines are from North Pole to South Pole. The coil is rotated at an angular speed,

$$\omega = 2 \pi n \text{ (rad/S)}$$

- N is rotating a rectangular coil in a counter clockwise direction with a angular velocity of ω radians per sec in a uniform magnetic field.
- The instant of coincidence of the plane of the coil with X-axis. At this instant max flux, Φ_{max} link with the coil
- The coil assume the position, as shown in fig , after moving the counter clockwise for t sec.
- The angle θ through which the coil has rotated in sec = ωt .

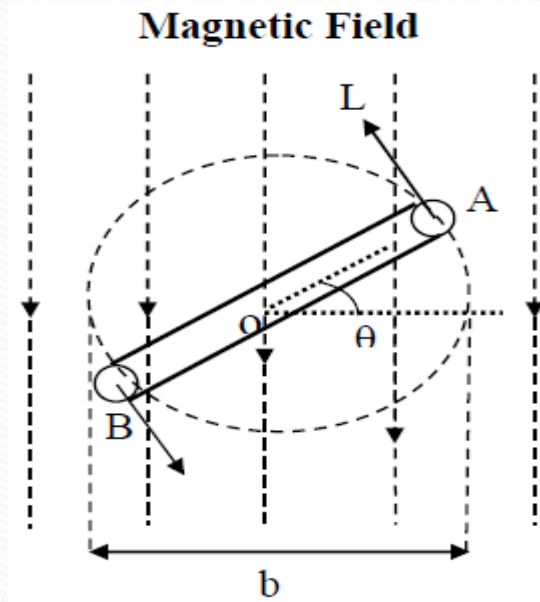

- The component of flux along perpendicular to the coil = $\Phi_{\max} \cos \omega t$.

- Flux linkage of the coil at the instant = no. of turns on coil \times linkage flux



$$N \Phi_{\max} \cos \omega t$$

- emf induced in a coil is equal to the rate of change of the flux linkage with minus sign .

- emf induced is max at any instant.


$$e = -\frac{d}{dt}[N\Phi_{\max}\cos \omega t] = N\Phi_{\max}\frac{d}{dt}[-\cos \omega t]$$
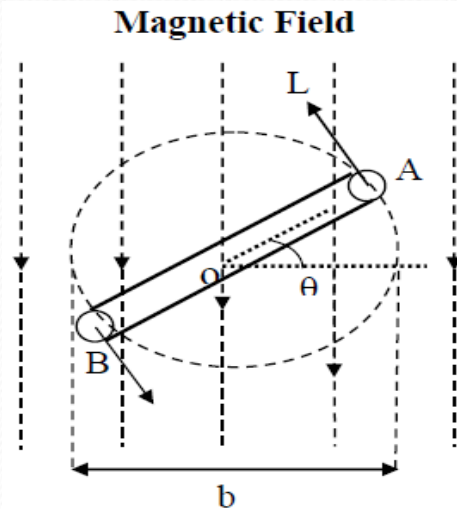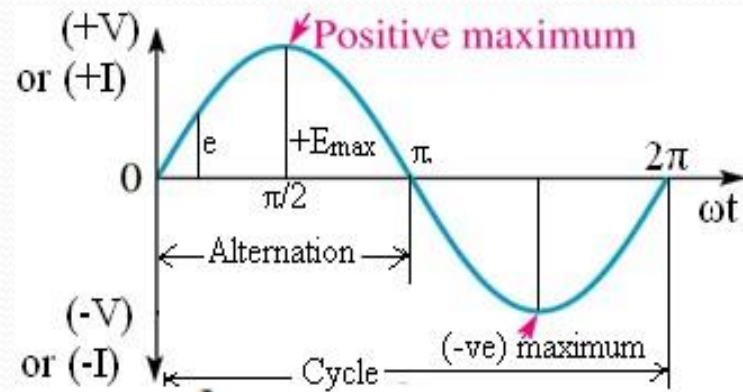
$$e = N\Phi_{\max} \omega \sin \omega t$$



- Instantaneous emf , $e = E_{\max} \sin \omega t$

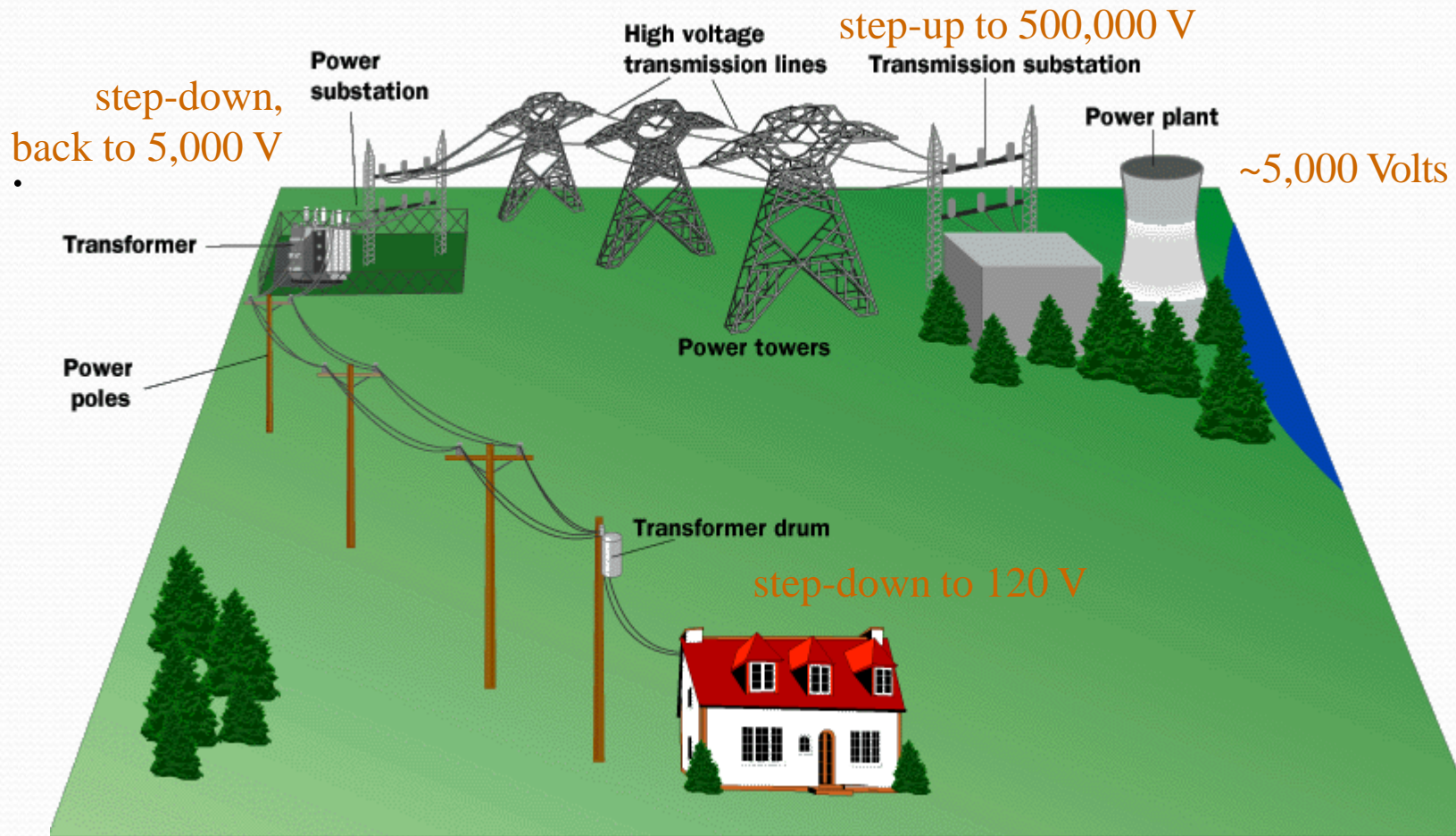A way to provide high efficiency, safe low voltage:



High Voltage Transmission Lines
Low Voltage to Consumers

Periodic Voltage or Current Waveform


● Average value

- The current waveform shown in Fig, is periodic in nature, with time period, T . It is positive for first half cycle, while it is negative for second half cycle.
- The average value of the waveform, $i(t)$ is defined as

$$I_{av} = \frac{\text{Area over half cycle}}{\text{Time period of half cycle}} = \frac{1}{T/2} \int_0^{T/2} i(t) dt = \frac{2}{T} \int_0^{T/2} i(t) dt$$

- In this case, only half cycle, or half of the time period, is to be used for computing the average value, as the average value of the waveform over full cycle is zero (0).
- If the half time period ($T/2$) is divided into 6 equal time intervals (ΔT)
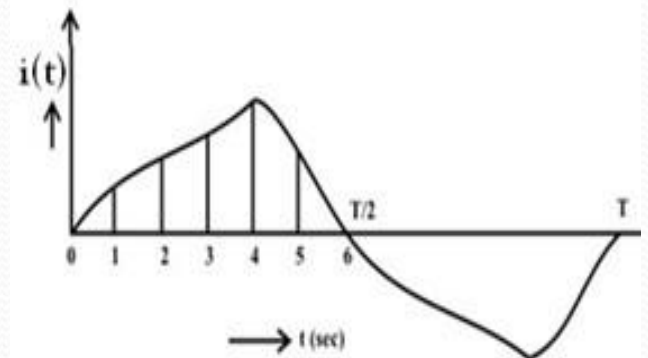
$$I_{av} = \frac{(i_1 + i_2 + i_3 + \dots i_6) \Delta T}{6 \cdot \Delta T} = \frac{(i_1 + i_2 + i_3 + \dots i_6)}{6}$$



Root Mean Square (RMS) value

- For this current in half time period subdivided into 6 time intervals as given above, in the resistance R, the average value of energy dissipated is given by



- Heat produce during interval = $I^2 R \frac{T}{n}$ joules

$$\propto \left[\frac{(i_1^2 + i_2^2 + i_3^2 + \dots + i_6^2)}{6} \right] R$$

$$I^2 R \Delta T = \left[\frac{(i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2) \Delta T}{n \cdot} \right] R$$

$$I = \sqrt{\frac{(i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2) \Delta T}{n \cdot \Delta T}} = \sqrt{\frac{\text{Area of } i^2 \text{ curve over half cycle}}{\text{Time period of half cycle}}}$$
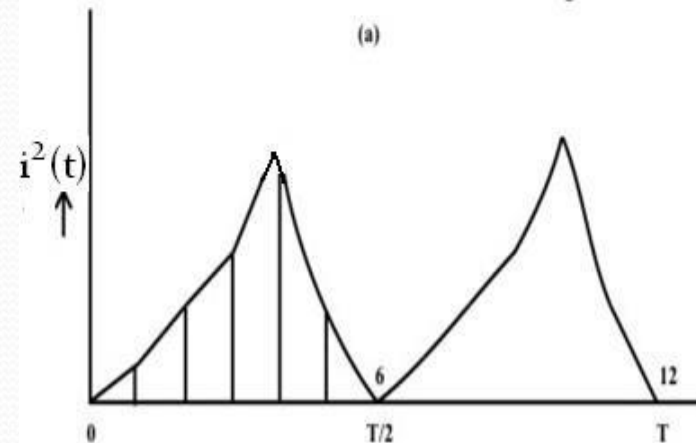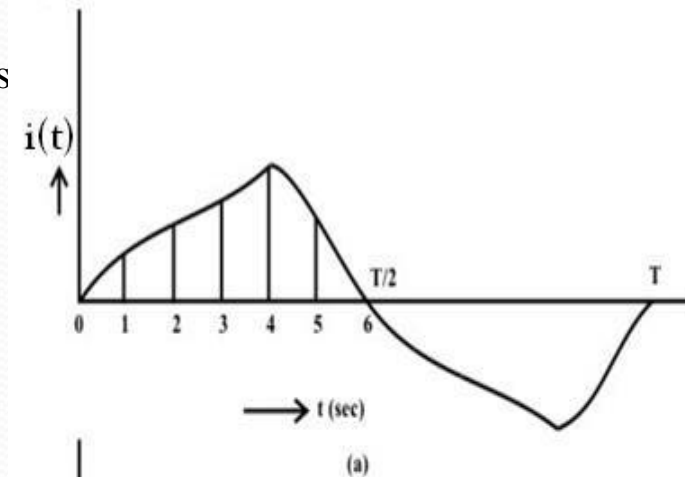
$$= \sqrt{\frac{1}{T/2} \int_0^{T/2} i^2 dt} = \sqrt{\frac{2}{T} \int_0^{T/2} i^2 dt}$$



Average Values of Sinusoidal Voltage Waveform

- The average value of sine wave over the complete cycle is zero.

- The half wave value of sinusoidal current is

$$I = I_{max} \sin \omega t$$

- For half cycle when ωt varies from 0 to π

$$I_{AV} = \frac{\text{area of half cycle}}{\pi}$$


$$I_{AV} = \frac{1}{\pi} \int_0^{\pi} i d(\omega t)$$

$$I_{AV} = \frac{1}{\pi} \int_0^{\pi} I_{max} \sin \omega t d(\omega t)$$

$$I_{AV} = \frac{I_{max}}{\pi} [-\cos \omega t] = \frac{2 I_{max}}{\pi} = 0.637 I_{max}$$

- Similarly
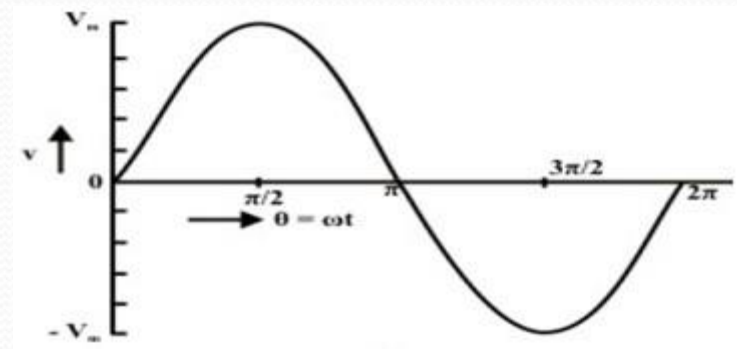
$$V_{AV} = \frac{2 V_{max}}{\pi} = 0.637 V_{max}$$



RMS Values of Sinusoidal Voltage Waveform

- The waveform of the voltage $v(t)$, and the square of waveform, $v^2(t)$, are shown in figures 12.4a and 12.4b respectively.

Time period, $T = 1/f = (2\pi)/\omega$; in angle ($\omega T = 2\pi$)

Half time period, $T/2 = 1/(2f) = \pi/\omega$; in angle ($\omega T/2 = \pi$)

$v(\theta) = V_m \sin \theta$ for $0 \leq \theta \leq 2\pi$;

$$V_{\text{rms}} = \left[\frac{1}{\pi} \int_0^\pi v^2 d\theta \right]^{\frac{1}{2}} = \left[\frac{1}{\pi} \int_0^\pi V_m^2 \sin^2 \theta d\theta \right]^{\frac{1}{2}} = \left[\frac{V_m^2}{\pi} \int_0^\pi \frac{1}{2} (1 - \cos 2\theta) d\theta \right]^{\frac{1}{2}}$$

$$V_{\text{rms}} = \left[\frac{V_m^2}{2\pi} \left(\theta - \frac{1}{2} \sin 2\theta \right) \Big|_0^\pi \right]^{\frac{1}{2}} = \left[\frac{V_m^2}{2\pi} \pi \right]^{\frac{1}{2}} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

$$\text{or, } V_m = \sqrt{2} V_{\text{rms}}$$

- Similarly for current RMA value

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} = 0.707 I_{\text{max}}$$

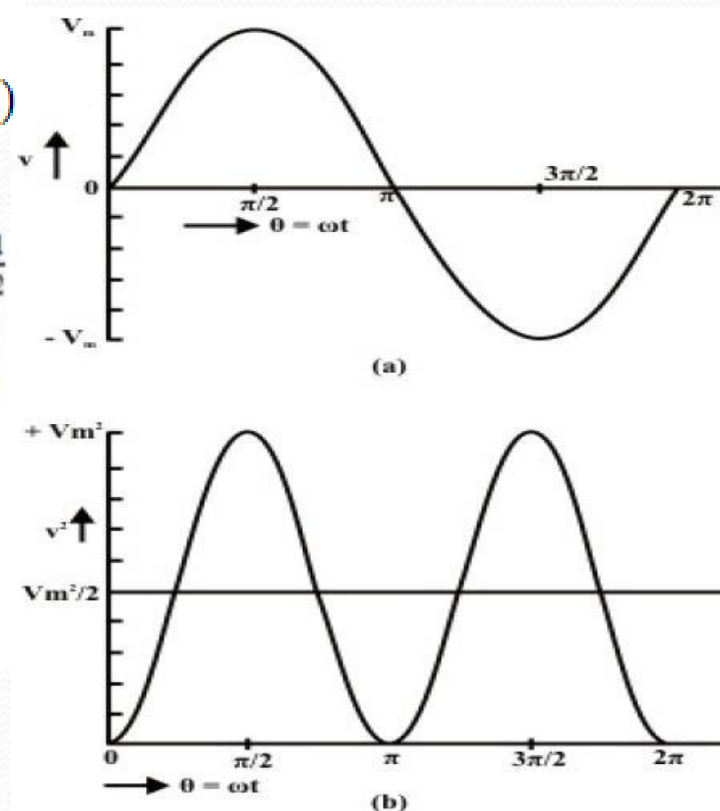


Fig. 12.4 Sinusoidal voltage waveform
(a) Voltage (v), (b) Square of voltage (v^2)

Form factors

- The form factor of an alternating quantity is define as the ratio of RMS value to the average value.

$$\text{Form factor} = \frac{\text{RMS value}}{\text{Average value}} = \frac{0.707 V_m}{0.637 V_m} = 1.11$$

- **Peak value:-**

- The peck factor of an alternating quantity is define as the ratio of maximum value to the average value

$$\begin{aligned}\text{Peak factor (P.E.)} &= \frac{\text{Maximum value}}{\text{RMS value}} \\ &= \frac{\text{Peak Value}}{\text{Peak Value}/\sqrt{2}} = \sqrt{2} \\ \text{P.F.} &= 1.414\end{aligned}$$

- **NOTE:-**

- The rms value is always greater than the average value.
- Except for a rectangular waveform, in which case the heating effect remains constant, so that the average and the rms values are same

Question

Q1) determine the average value and RMS value of sinusoidal current of peak value 40A.

Solution:- $I_{max} = 40A$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$I_{av} = 0.637 I_{max}$$

Q2) write the instantaneous value for a 50Hz sinusoidal voltage supply for domestic purposes at 230V.

Solution:- given value $V_{rms} = 230 V$, $f = 50 \text{ Hz}$

$$V(t) = V_{max} \sin \omega t$$

$$V_{max} = \sqrt{2} \times V_{rms}$$

$$\omega = 2\pi f$$

Single-phase AC Supply




- Purely resistive circuit (R only)

- The instantaneous value of the current through the circuit is given by

$$v = V_m \sin \omega t$$

- I_m and V_m are the maximum values of current and voltage respectively
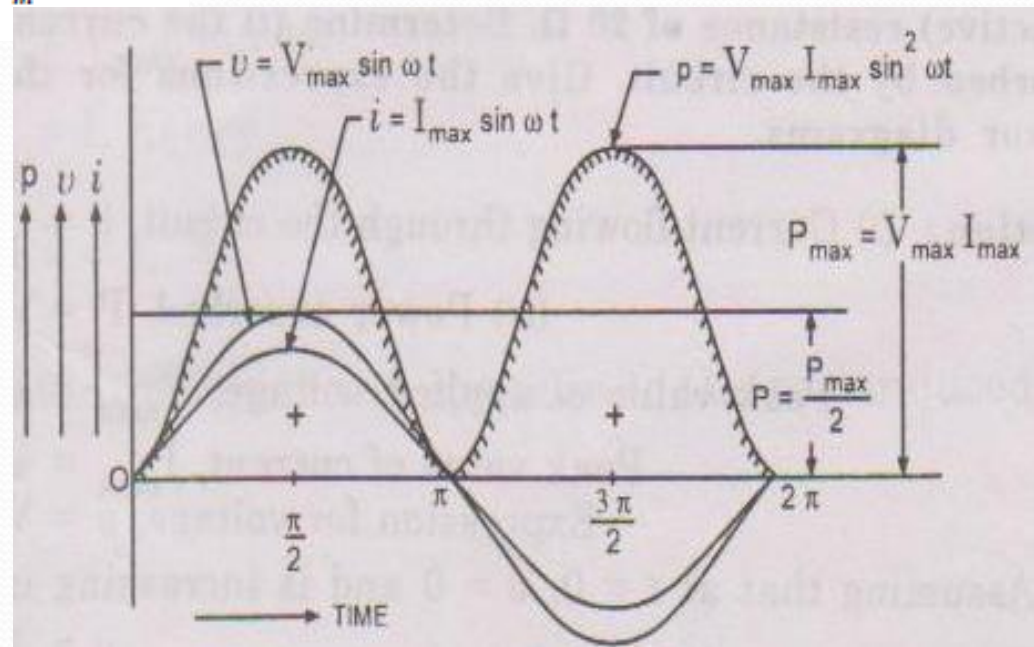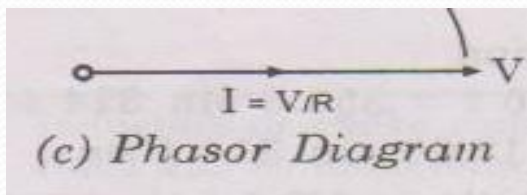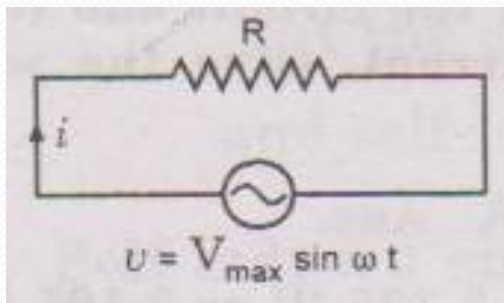
$$i = \frac{v}{R} = \frac{V_m}{R} \sin \omega t = I_m \sin \omega t$$



Purely inductive circuit (L only)

- For the circuit, the current i , is obtained by the procedure described here




$$\text{As } v = L \frac{di}{dt} = V_m \sin \omega t$$

$$di = \frac{V}{L} \sin(\omega t) dt$$

Integrating,

$$i = -\frac{V_m}{\omega L} \cos \omega t = \frac{V_m}{\omega L} \sin(\omega t - 90^\circ)$$

$$= I_m \sin(\omega t - 90^\circ)$$

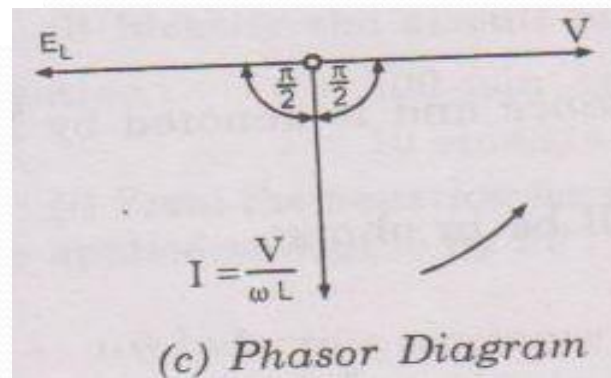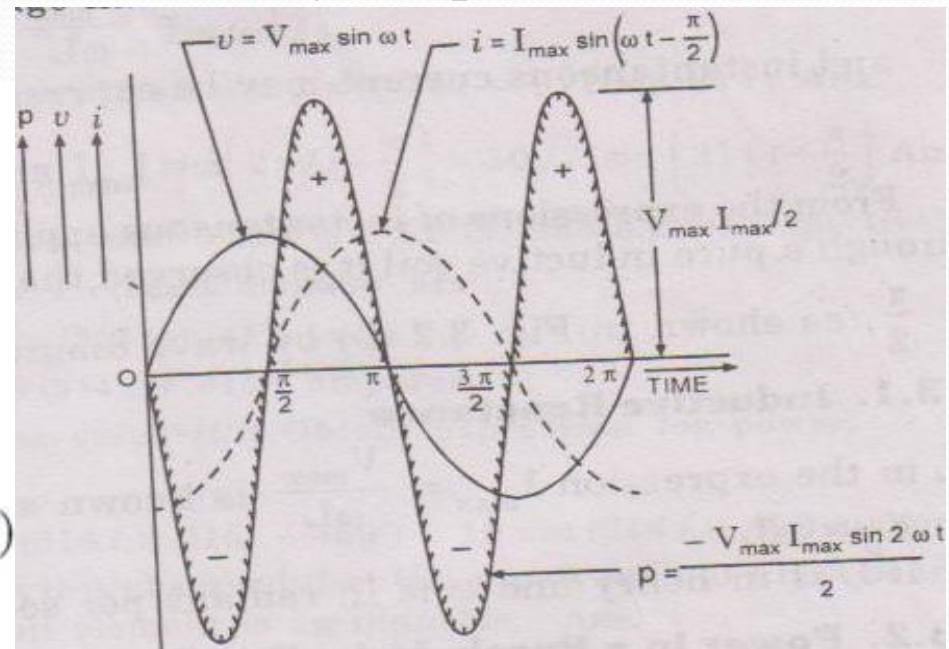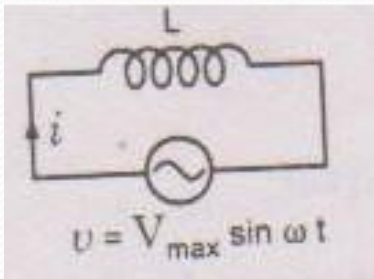

Purely capacitive circuit (C only)

The current i , in the circuit (Fig. 14.3a), is,




$$i = C \frac{dv}{dt}$$

Substituting $v = V_m \sin \omega t$, i is

$$i = C \frac{d}{dt} (V_m \sin \omega t) = \omega C V_m \cos \omega t$$

$$= \omega C V_m \sin(\omega t + 90^\circ)$$

$$= I_m \sin(\omega t + 90^\circ)$$

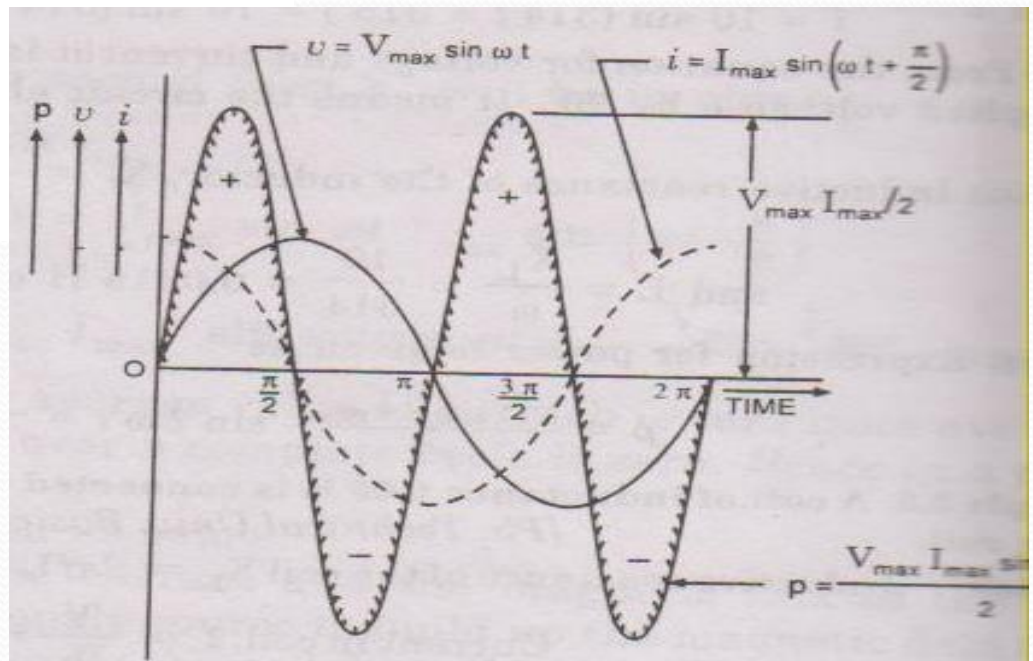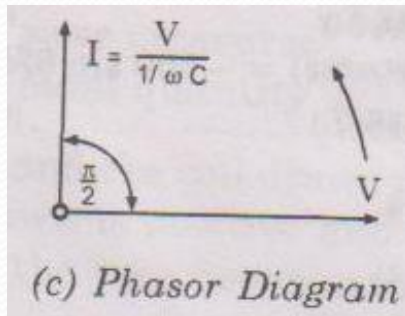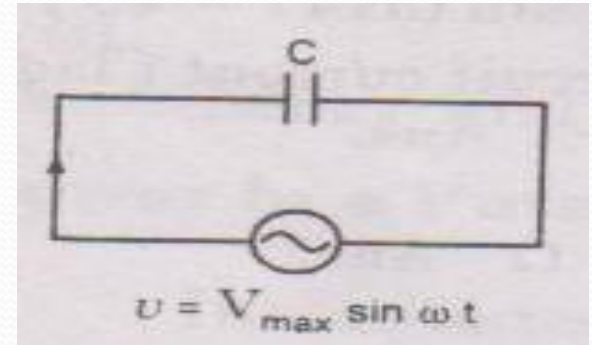

- From our earlier discussions we know that

$$v = V_m \sin(\omega t + \phi)$$

where V_m is the **peak voltage**


ω is the **angular frequency**

ϕ is the **phase angle**


- Since $\omega = 2\pi f$ it follows that the period T is given by

$$T = \frac{1}{f} = \frac{2\pi}{\omega}$$

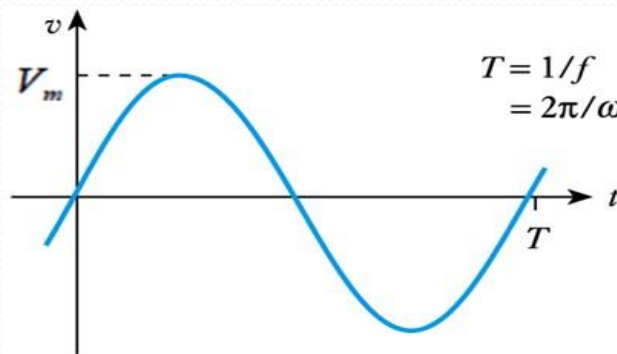- If ϕ is in radians, then a time delay t is given by ϕ / ω as shown below




(a) $v = V_m \sin(\omega t)$

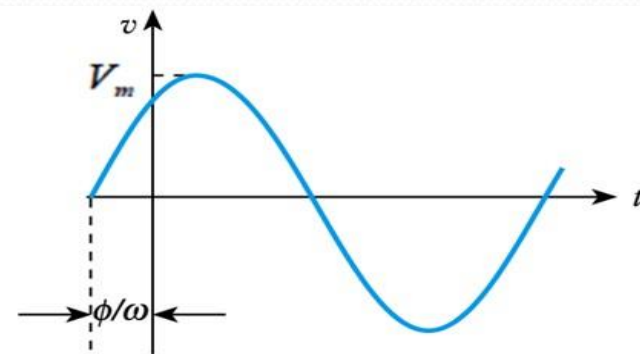


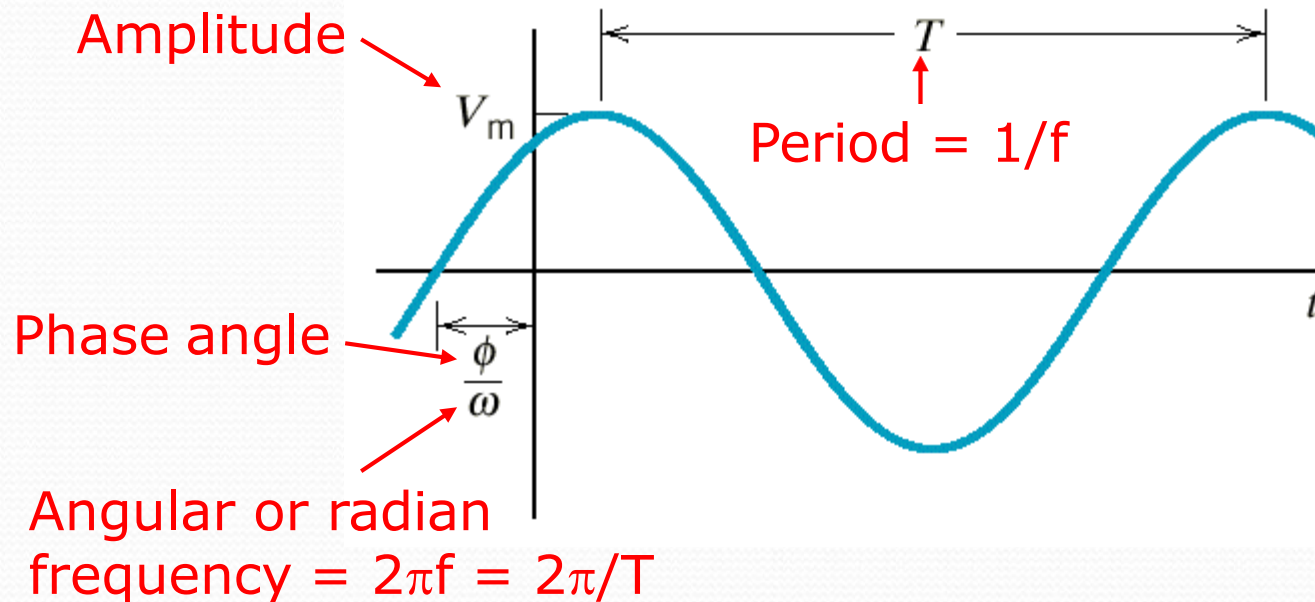(b) $v = V_m \sin(\omega t + \phi)$

- Sinusoidal signals are characterised by their **magnitude**, their **frequency** and their **phase**




Example

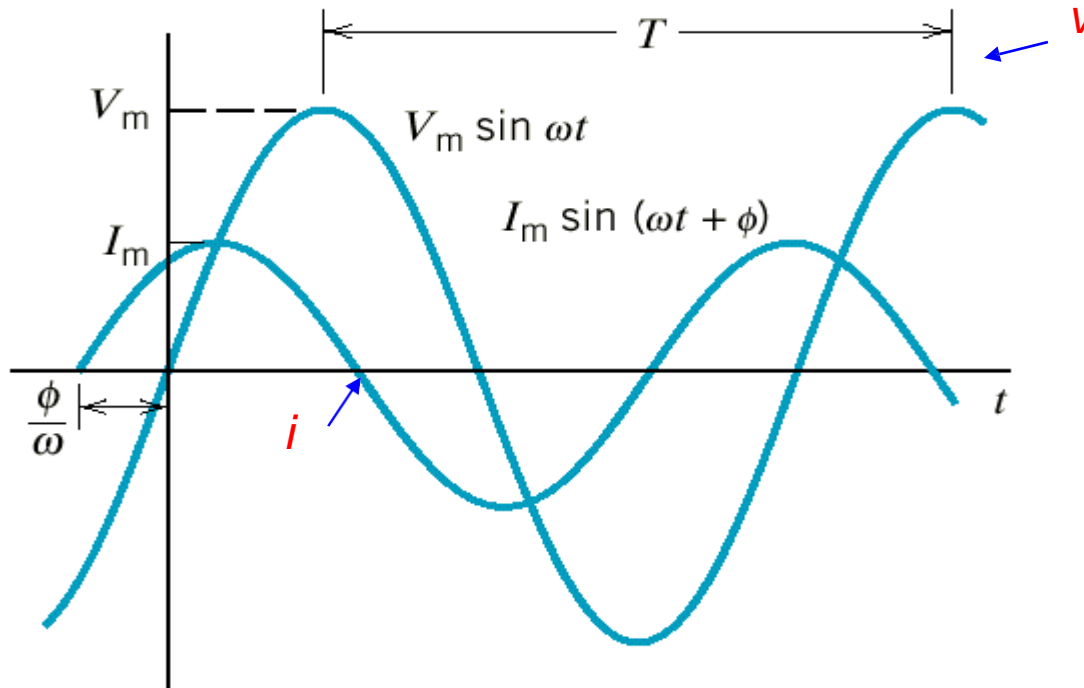

Voltage and current of a circuit element.

$$\cos \theta = \sin \left(\theta + \frac{\pi}{2} \right)$$
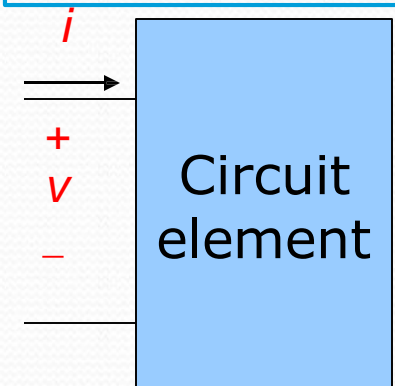
$$\sin \theta = \cos \left(\theta - \frac{\pi}{2} \right)$$



The current *leads* the voltage by ϕ radians.

OR

The voltage *lags* the current by ϕ radians.

Mathematical representation of phasor

- Phasor can be representation in two way.

- Rectangular form
- Polar form

Polar form:-

- The instantaneous voltage $v_s = V_m \sin(\omega t + \phi)$ can be represented in polar form.

$$\mathbf{v}_s = V_m \angle \phi$$

- For example $v(t) = 20 \sin(2\pi ft + 60)$.
- Then it represented in the polar form

$$v(t) = 20 \angle 60^\circ \text{ volt}$$

For Rectangular form:-

- The instantaneous voltage $v_s = V_m \sin(\omega t + \phi)$ can be represented in Rectangular form.

$$v(t) = x + jy$$

Where 'x' is x component of the phasor $= V_m \cos \phi$

'y' is y component of the phasor $= V_m \sin \phi$

- $V(t) = V_m \cos \phi + j V_m \sin \phi$

Example: $v(t) = 20 \sin(2\pi ft + 60)$.

$$v(t) = 20 \angle 60^\circ \text{ volt}$$

$$v(t) = 20 (\cos 60 + j \sin 60) = (10 + j17.32)$$

Conversion from polar to rectangular:

- Polar form : $\mathbf{v}_s = r \angle \phi$
- For x component $x = r \cos \phi$ and y component $y = r \sin \phi$
- $v(t) = x + jy$
- $V(t) = r \cos \phi + j r \sin \phi$

Conversion from rectangular to polar :

- For rectangular form $v(t) = x + jy$

$$r^2 = x^2 + y^2$$


$$r = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1} \left(\frac{y}{x} \right)$$

- For polar form $\mathbf{v}_s = r \angle \phi = \sqrt{x^2 + y^2} \angle \tan^{-1} \left(\frac{y}{x} \right)$

Phasor Relationship for R, L, and C Elements

Time domain


$$v = Ri$$

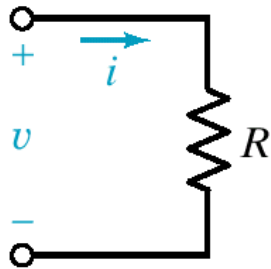

(a)


Frequency domain
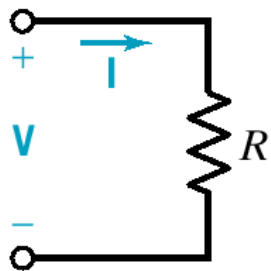
$$\mathbf{V} = R\mathbf{I} \quad \text{or} \quad \mathbf{I} = \frac{\mathbf{V}}{R}$$




(b)

Resistor

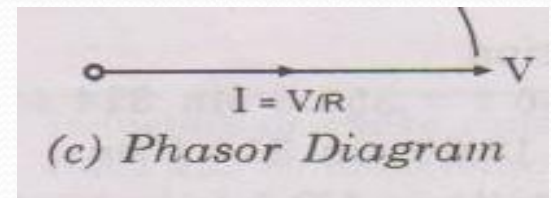

Voltage and current are *in phase*.


Inductor

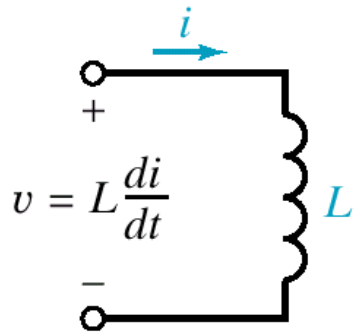

(a)

Time domain

$$v = L \frac{di}{dt}$$

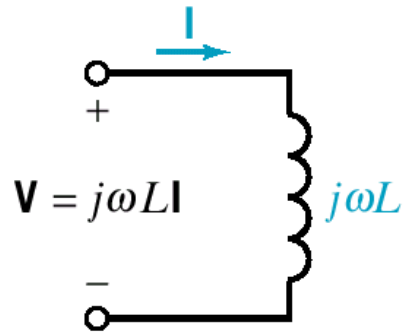

(b)

Frequency domain

$$\mathbf{V} = j\omega L \mathbf{I} \quad \text{or} \quad \mathbf{I} = \frac{\mathbf{V}}{j\omega L} = \frac{-j\mathbf{V}}{\omega L}$$

Voltage *leads* current by 90°


Current *lags* voltage by 90°

$$\text{As } v = L \frac{di}{dt} = V_m \sin \omega t$$


$$di = \frac{V}{L} \sin(\omega t) dt$$

$$i = -\frac{V_m}{\omega L} \cos \omega t = \frac{V_m}{\omega L} \sin(\omega t - 90^\circ)$$


$$= I_m \sin(\omega t - 90^\circ)$$

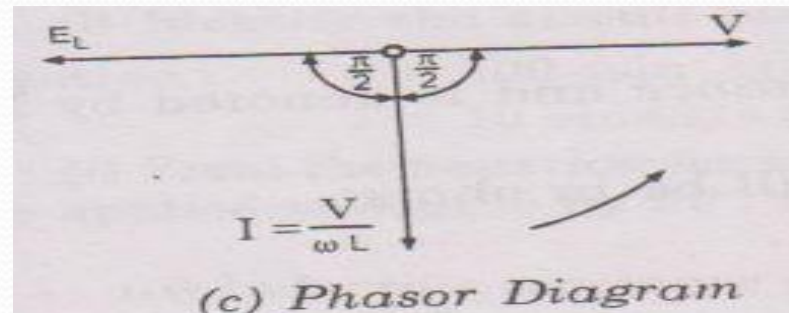

Capacitor

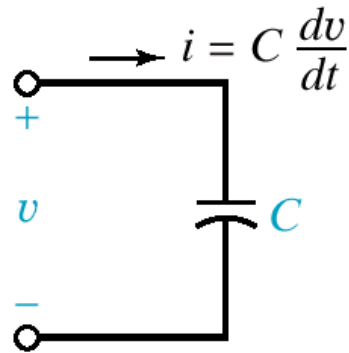

(a)

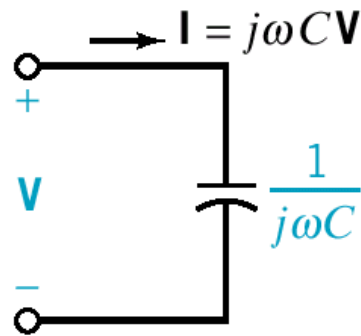

(b)

The current i , in the circuit

$$i = C \frac{dv}{dt}$$

$$\begin{aligned} i &= C \frac{d}{dt} (V_m \sin \omega t) = \omega C V_m \cos \omega t \\ &= \omega C V_m \sin(\omega t + 90^\circ) \\ &= I_m \sin(\omega t + 90^\circ) \end{aligned}$$

Time domain


$$V = \frac{1}{C} \int i(t) dt$$

$$i = C \frac{dv}{dt}$$

Frequency domain

$$I = j\omega CV \quad \text{or} \quad V = \frac{I}{j\omega C} = \frac{-jI}{\omega C}$$

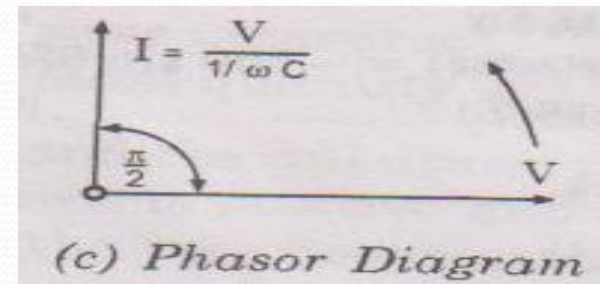Voltage lags current by 90°
Current leads voltage by 90°



(c) Phasor Diagram

Impedance and Admittance

Impedance is defined as the ratio of the **phasor voltage** to the **phasor current**.

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}}$$

Ohm's law in phasor notation

$$= \frac{V_m \angle \phi}{I_m \angle \beta} = \frac{V_m}{I_m} \angle \phi - \beta$$

phase $\theta = \phi - \beta$


magnitude $|\mathbf{Z}|$

or

$$\mathbf{Z} = |\mathbf{Z}| \angle \theta = Ze^{j\theta} = R + jX$$

polar exponential rectangular

Graphical Representation of Impedance

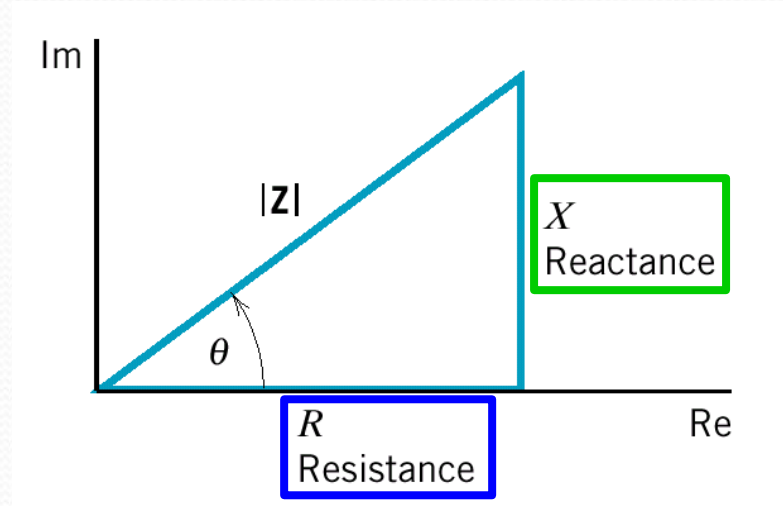


$$\mathbf{Z} = |\mathbf{Z}| \angle \theta$$

$$|\mathbf{Z}| = \sqrt{R^2 + X^2}$$

$$\theta = \tan^{-1} \frac{X}{R}$$


Resistor

$$\mathbf{Z} = R$$

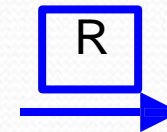


Inductor

$$\mathbf{Z} = j\omega L$$

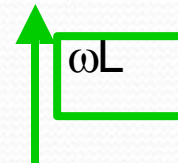

Capacitor
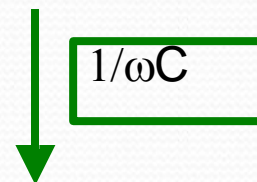
$$\mathbf{Z} = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$



Admittance is defined as the reciprocal of **impedance**.

In Polar form

$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = \frac{1}{|\mathbf{Z}| \angle \theta} = |\mathbf{Y}| \angle -\theta$$

In rectangular form


$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2} = G + jB$$

conductance

susceptance

Resistor

$$\mathbf{Y} = G = \frac{1}{R}$$

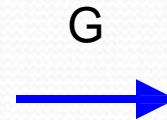

Inductor

$$\mathbf{Y} = \frac{1}{j\omega L}$$

$1/\omega L$



Capacitor

$$\mathbf{Y} = j\omega C$$


ωC



AC circuit with series element

● The series R-L Circuit

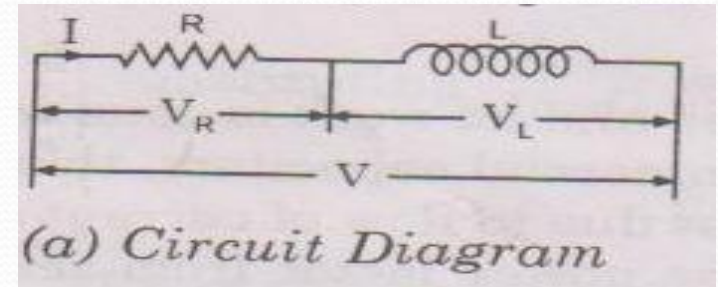- We consider the ac circuit consisting of resistance of R and inductance of L connecting in series.



$$V = V_R + V_L$$

$$V_R = I R$$

$$V_L = I X_L$$

$$V = I R + I X_L \quad \text{where } X_L = \omega L = 2\pi f L$$


- Vector sum of the V_R and V_L

$$V = \sqrt{V_R^2 + V_L^2} \quad V = \sqrt{(IR)^2 + (IX_L)^2}$$

$$V = \sqrt{I^2(R^2 + X_L^2)} = I\sqrt{(R^2 + X_L^2)}$$

$$|Z| = \sqrt{(R^2 + X_L^2)} = \text{Impedance of the circuit}$$

$$V = I |Z| \quad \phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

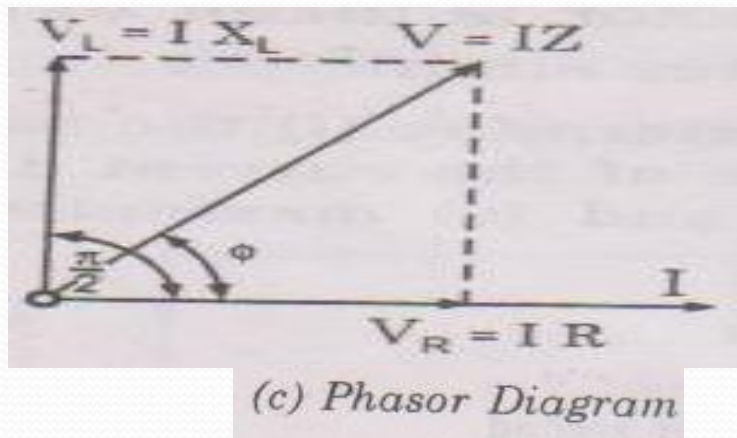

Impedance of R-L series circuit

- Impedance of R-L series circuit is expressed in the rectangular form as

- $Z = R + j X_L$

- Expressed in the polar form as

$$\mathbf{Z} = |\mathbf{Z}| \angle \phi \quad \phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$|Z| = \sqrt{(R^2 + X_L^2)} = \text{Impedance of the circuit}$$


- Expression for current:

- The current through the R-L circuit is


$$i(t) = \frac{V(t)}{Z} = \frac{V \angle \phi}{|Z| \angle \phi} = \frac{V \angle -\phi}{|Z|}$$

- $i(t) = I_m \angle -\phi$ Amp.

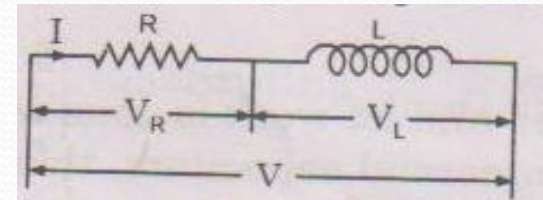- instantaneous current $i(t) = I_m \sin (\omega t - \phi)$



(a) Circuit Diagram

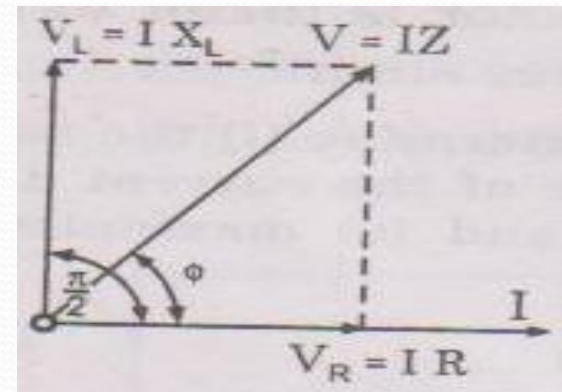

Let $\frac{V}{|Z|} = I_m$

Power in Resistance - inductance circuit

- Instantaneous power,

$$P = v i = V_{max} \sin \omega t \times I_{max} \sin(\omega t - \phi)$$

$$= \frac{1}{2} V_{max} \times I_{max} [2 \sin \omega t \cdot \sin(\omega t - \phi)]$$

$$= \frac{1}{2} V_{max} \times I_{max} [\cos \phi - \cos(2\omega t - \phi)]$$

$$= \frac{1}{2} V_{max} I_{max} \cos \phi - \frac{1}{2} V_{max} I_{max} \cos(2\omega t - \phi)$$



- Since average value of pulsating component $\frac{1}{2} V_{max} I_{max} \cos(2\omega t - \phi)$ over the complete cycle is zero.

- The average power of the circuit

$$P = \text{constnt component} = \frac{1}{2} V_{max} I_{max} \cos \phi$$



$$= \frac{V_{max}}{\sqrt{2}} \frac{I_{max}}{\sqrt{2}} \cos \phi = VI \cos \phi$$

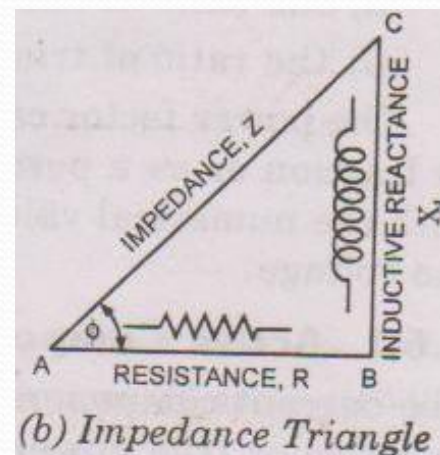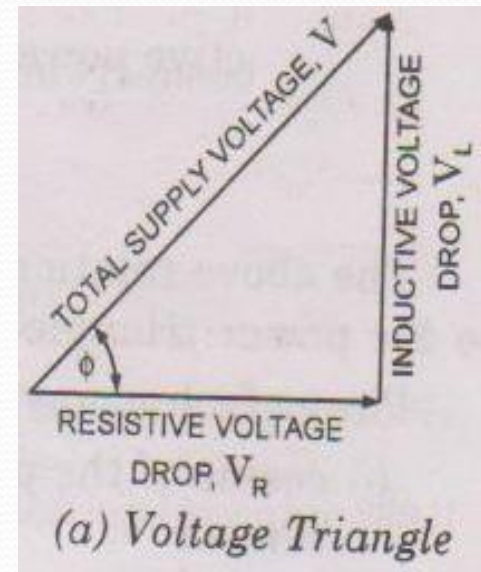- V & I are the RMS value of voltage & current and ϕ is the phase angle between applied voltage & current.



The series R-C Circuit

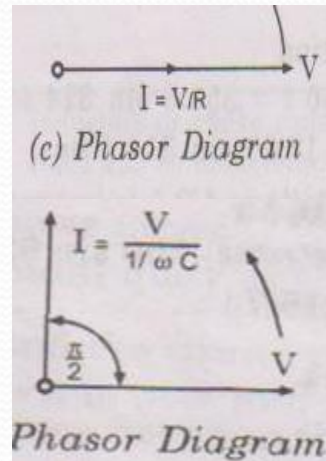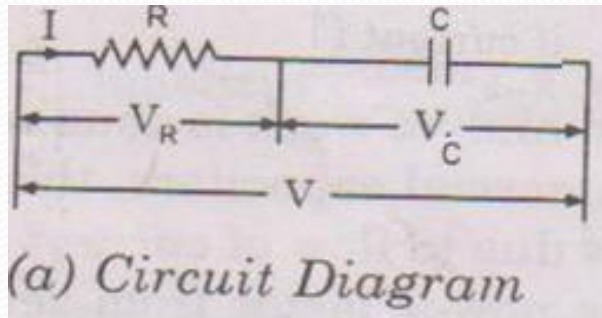- We consider the ac circuit consisting of resistance of R and inductance of L connecting in series



- Voltage drop across R , $V_R = I R$
(V_R is in phase with I)
- Voltage drop across C , $V_C = I X_C$
(V_C lags I by 90°)


Applying KVL for RC series circuit

$$V = V_R + V_C$$

$$V_R = I R \text{ and } V_C = I X_C$$

$$V = I R + I X_C \quad \text{where } X_C = 1/\omega C = 1/2\pi f C$$

Vector sum of V_R and V_L

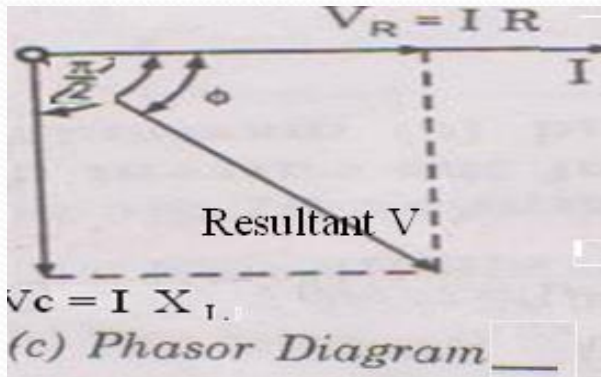

$$V = \sqrt{V_R^2 + V_C^2} \quad V = \sqrt{(IR)^2 + (IX_C)^2}$$

$$V = \sqrt{I^2(R^2 + X_C^2)} = I\sqrt{(R^2 + X_C^2)}$$

$$|Z| = \sqrt{(R^2 + X_C^2)} = \text{Impedance of the circuit}$$

$$V = I |Z|$$

Impedance of R-C series circuit

- Impedance of R-C series circuit is expressed in the rectangular form as

- $Z = R - j X_c$

- Expressed in the polar form as

$$\mathbf{Z} = |\mathbf{Z}| \angle \phi \quad \phi = \tan^{-1} \left(\frac{-X_c}{R} \right)$$

$$|Z| = \sqrt{(R^2 + X_c^2)} = \text{Impedance of the circuit}$$

- Expression for current:




- The current through the R-L circuit is

$$i(t) = \frac{V(t)}{Z} = \frac{V \angle \phi}{|Z| \angle -\phi} = \frac{V \angle \phi}{|Z|}$$

$$\text{Let } \frac{V}{|Z|} = I_m$$


- $i(t) = I_m \angle \phi$ Amp.

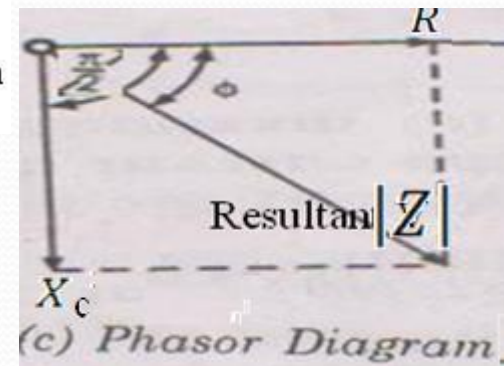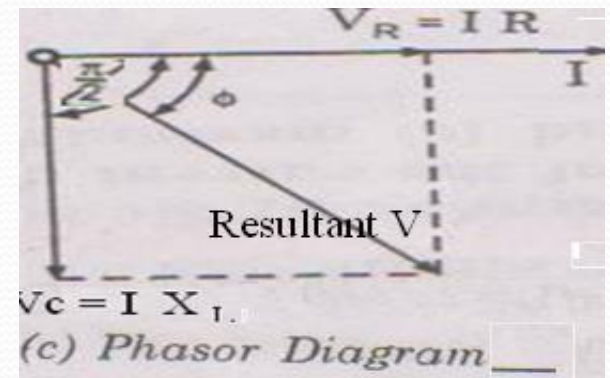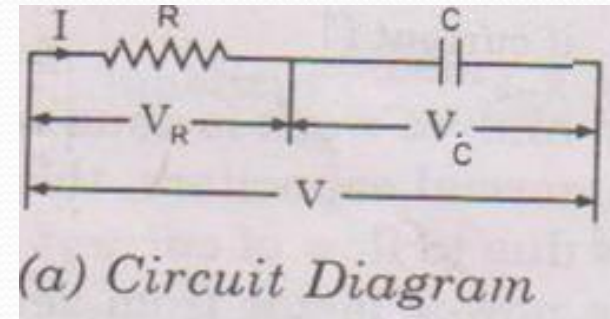- instantaneous current $i(t) = I_m \sin(\omega t + \phi)$




Series R-L-C Circuit

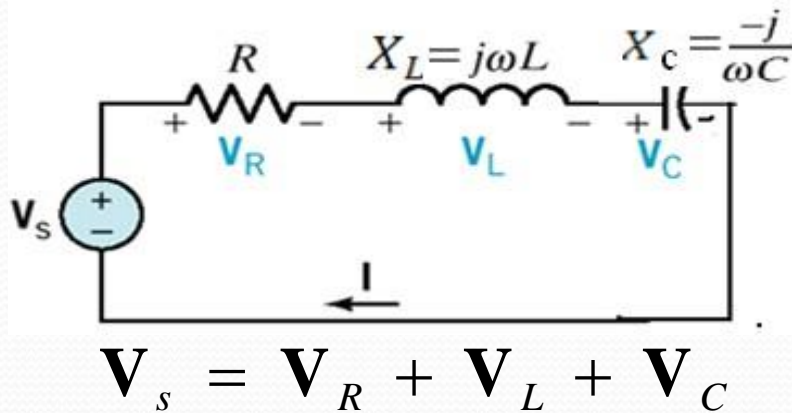A **Phasor Diagram** is a graphical representation of phasors and their relationship on the *complex plane*.



The voltage phasors are
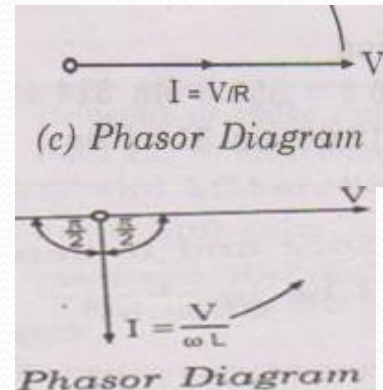
$$\begin{cases} \mathbf{V}_R = R\mathbf{I} = RI \angle 0^\circ \\ \mathbf{V}_L = j\omega L\mathbf{I} = \omega LI \angle 90^\circ \\ \mathbf{V}_C = \frac{-j}{\omega C}\mathbf{I} = \frac{I}{\omega C} \angle -90^\circ \end{cases}$$





- Applied voltage V , being equal to the phasor vector sum of V_R , V_L & V_C is given in magnitude

$$\begin{aligned} V &= \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(IR)^2 + (IX_L - IX_C)^2} \\ &= I\sqrt{(R)^2 + (X_L - X_C)^2} \end{aligned}$$




$$|Z| = \sqrt{(R)^2 + (X_L - X_C)^2} = \text{Impedance of the circuit}$$

$$V = I |Z| \quad \phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

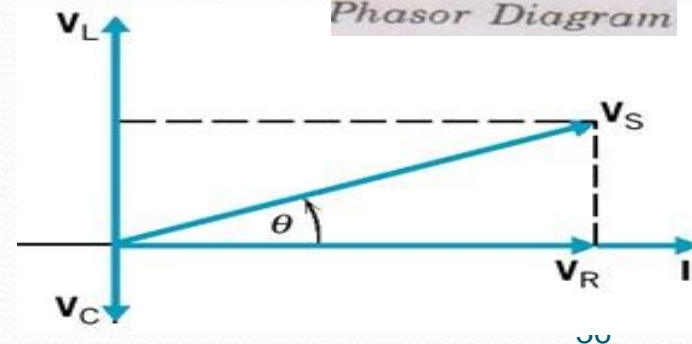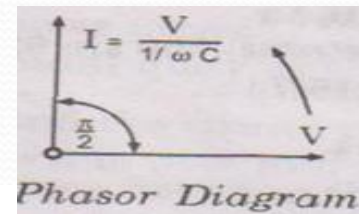




Three-phase System

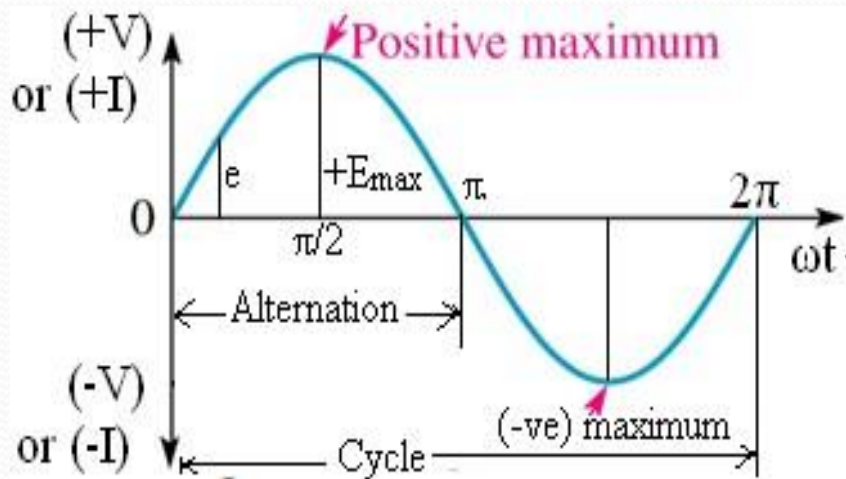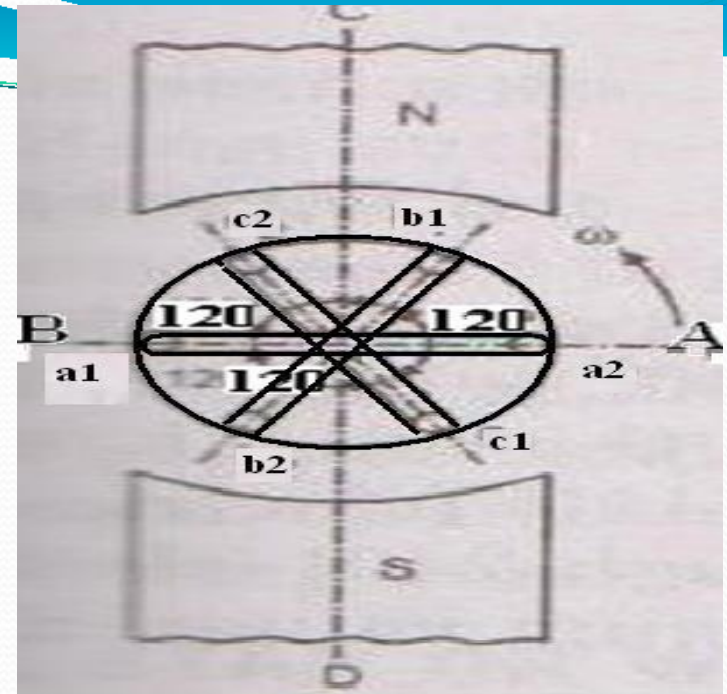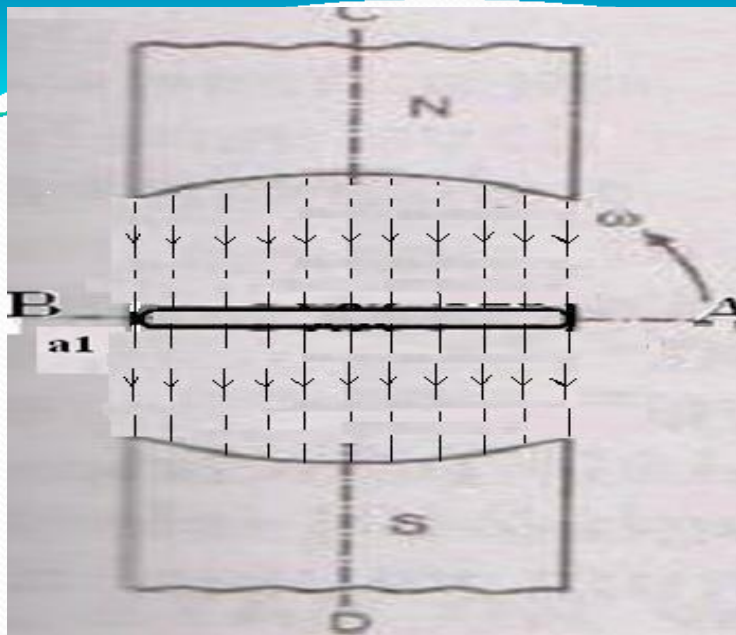

● Single phase generator

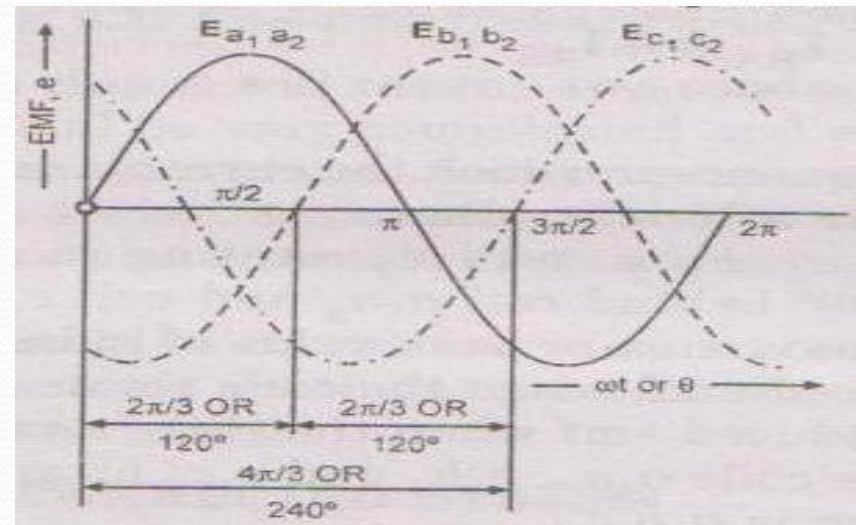

● Three phase generator


Three-phase AC Circuits

● Generation of Three-phase Balanced Voltages



- Three windings, with equal no. of turns in each one, are used, so as to obtain **equal voltage in magnitude** in all three phases.
- Also to obtain a balanced three-phase voltage, the windings are to be placed at an electrical angle of 120 with each other.

● Construction:-

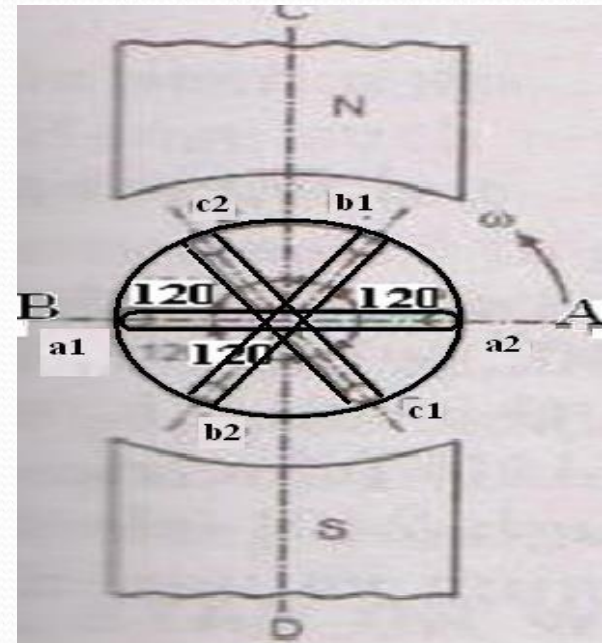- consider three identical coil “a1a2”, “b1 b2”, and “c1c2” are mounted in same axis but displaced from each other by 120 rotating in counter clockwise direction in bipolar magnetic field as shown in fig.



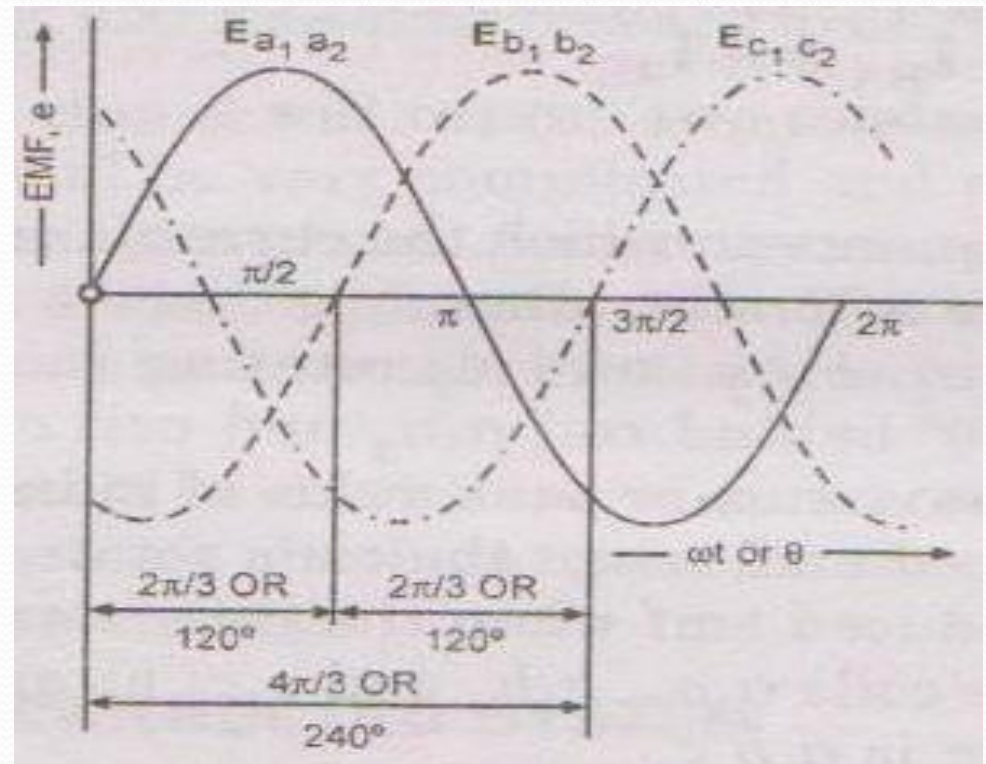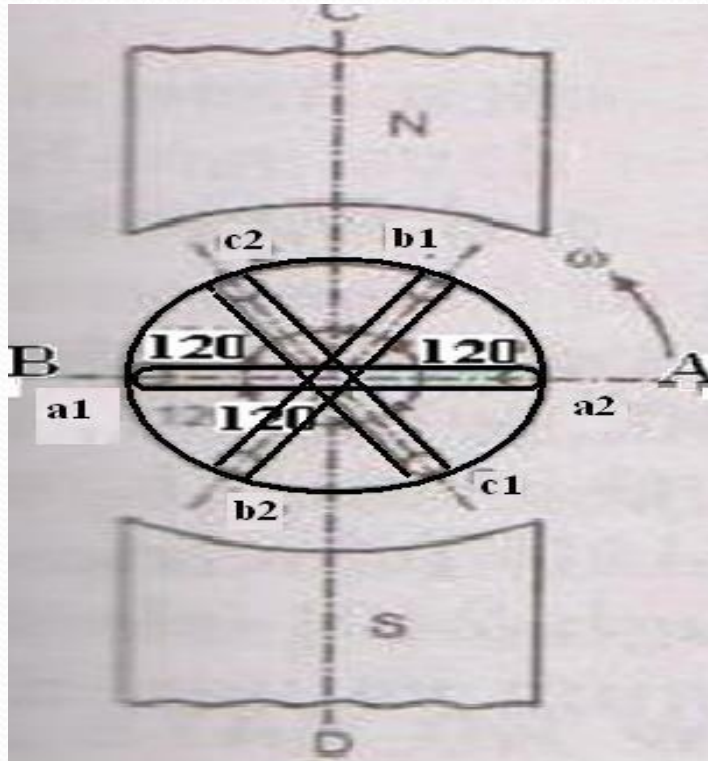- When a coil “a1 a2” is the position AB the induced emf in this coil is zero.
- At that time ‘b1 b2’ is 120° behind the coil ‘a1 a2’ so the emf is induced in this coil as approaching its maximum negative (-ve) value .
- At the same time ‘c1 c2’ is 240° behind the coil ‘a1 a2’ so the emf is induced in this coil as approaching its maximum positive (+ve) value and is decreasing



Some important point


- The induced emf in each of the coil are of same magnitude.
- The induced emf in each of the coil are of same frequency and Waveform (sinusoidal wave).
- The instantaneous value of the emf induced in the coil “a1 a2” , “b1 b2” and “ c1 c2”is given as below.

$$e_{a_1 a_2} = E_{max} \sin \omega t$$

$$e_{b_1 b_2} = E_{max} \sin(\omega t - 120^\circ)$$

$$\begin{aligned} e_{c_1 c_2} &= E_{max} \sin(\omega t - 240^\circ) \\ &= E_{max} \sin(\omega t + 120^\circ) \end{aligned}$$

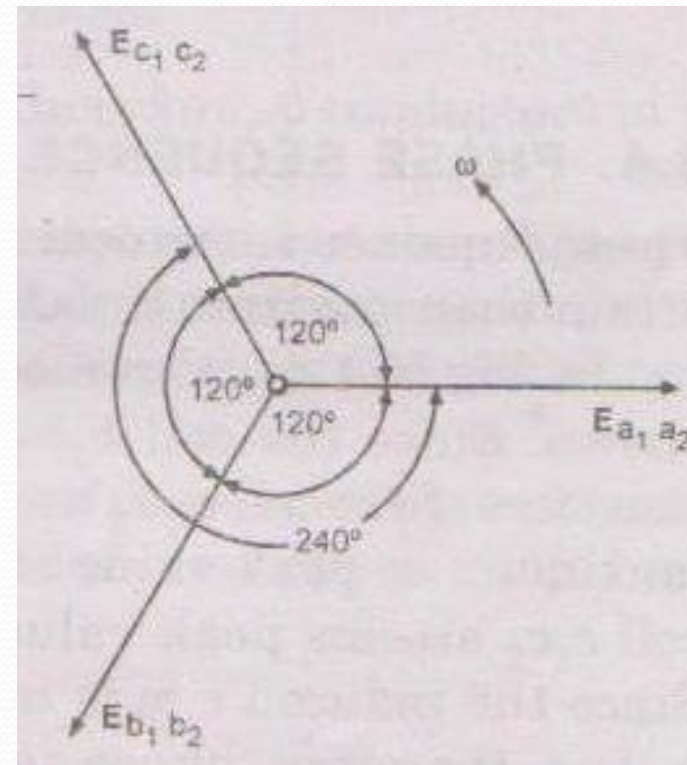- Note:- if $t = 0$ corresponding to the instant then voltage & emf of the coil “a1 a2” pass through zero & increasing in positive direction.



Balance Three Phase Star Connection

- The connection diagram of a star (Y)-connected three-phase system is shown in Fig.
- Three phase voltages (E_P) are:

$$e_{RN} = E_m \sin \theta; \quad e_{YN} = E_m \sin (\theta - 120^\circ);$$

$$e_{BN} = E_m \sin (\theta - 240^\circ) = E_m \sin (\theta + 120^\circ)$$

$$E_{RN} \angle 0^\circ = E (1.0 + j0.0):$$

$$E_{YN} \angle -120^\circ = E (-0.5 - j0.866);$$


$$E_{BN} \angle +120^\circ = E (-0.5 + j0.866).$$

- Three line voltages (E_L) are:




- E_{RY}

- E_{RB}

- E_{YB}

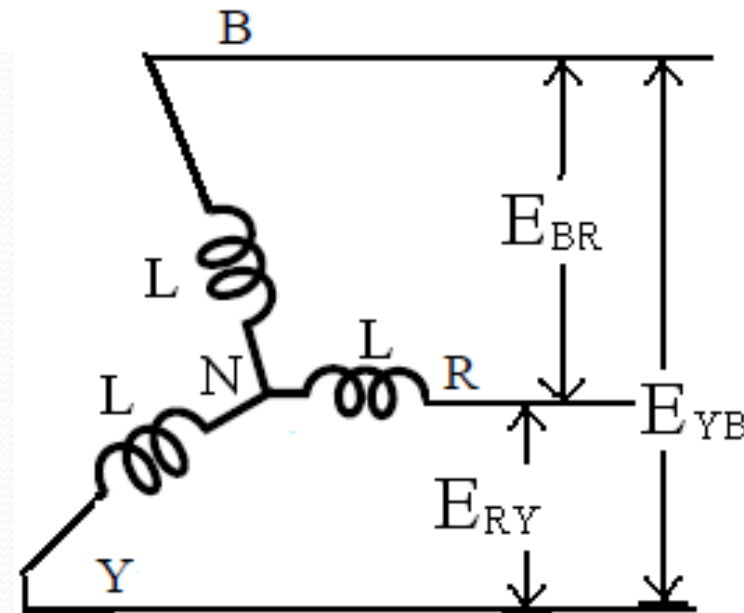

Phase Representation of Star Connection

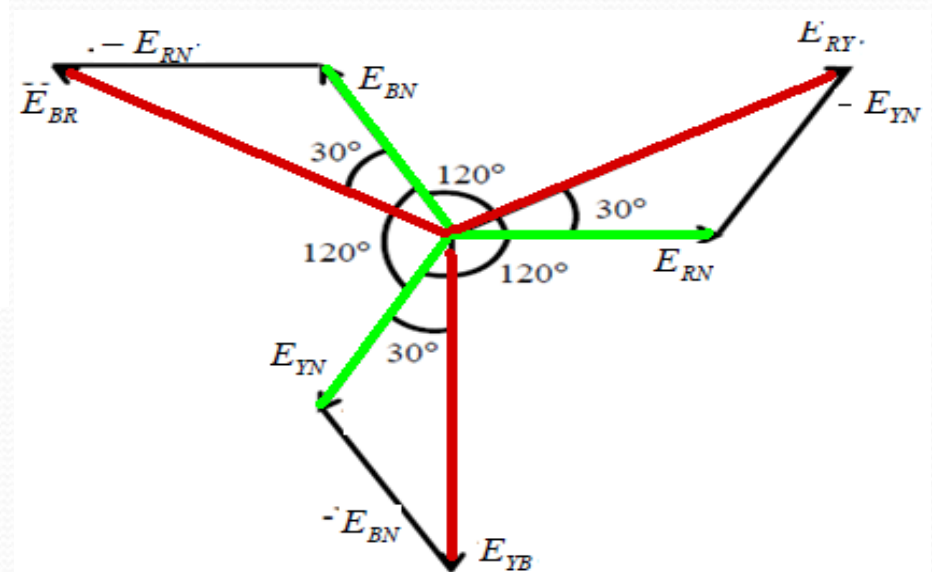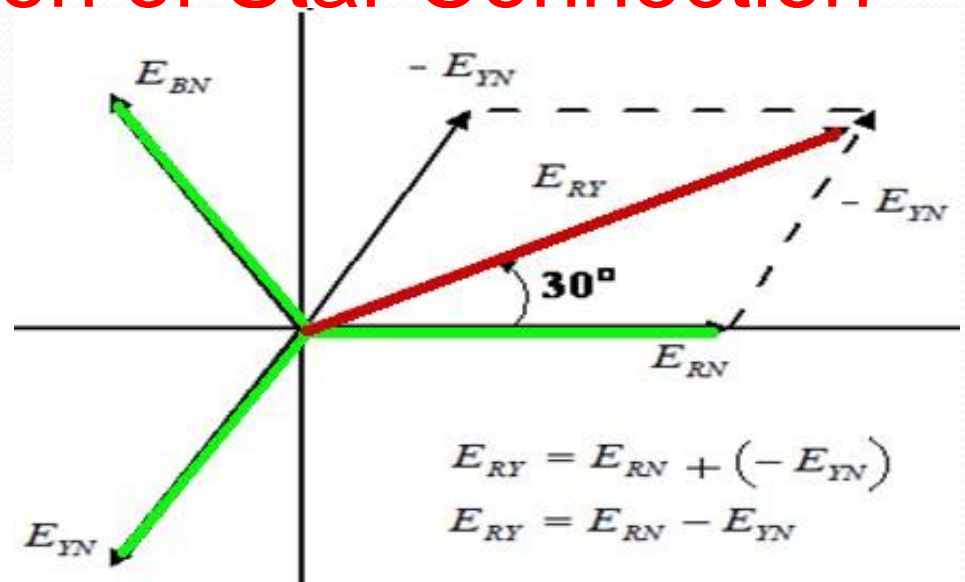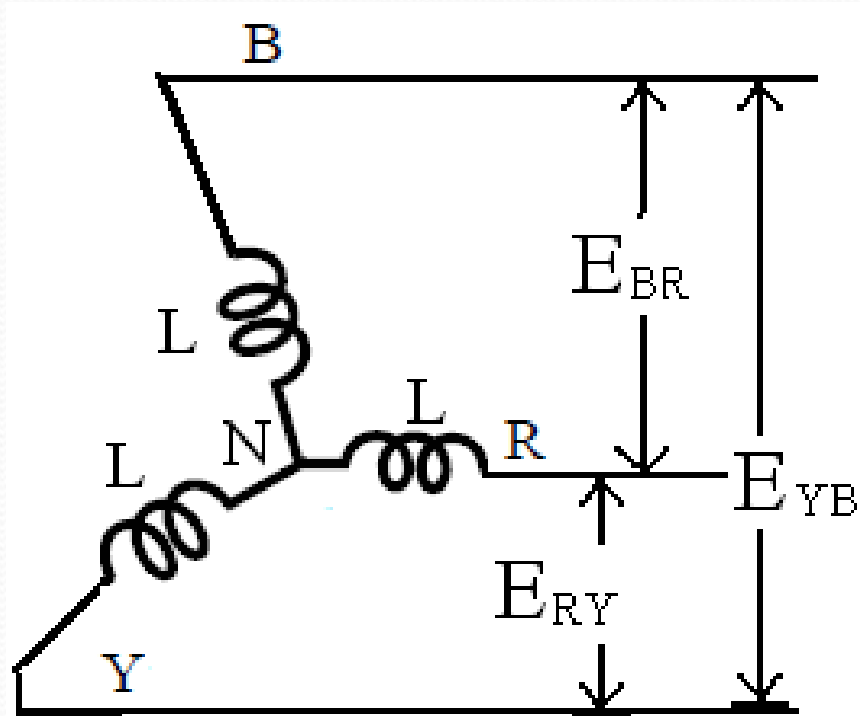

Relation between Phase and Line Voltages for Star Connection

- Three line voltages are obtained by the following procedure. The line voltage, E_{RY} is

$$E_{RY} = E_{RN} - E_{YN} = E \angle 0^\circ - E \angle -120^\circ$$


$$= E [(1 + j0) - (-0.5 - j0.866)]$$

$$= E (1.5 + j0.866) = \sqrt{3} E \angle 30^\circ$$

$$E_L = E_{RY} = \sqrt{3} E \angle 30^\circ = \sqrt{3} E_P \angle 30^\circ$$

- The magnitude of the line voltage, E_{RY} is $\sqrt{3}$ times the magnitude of the phase voltage E_{RN} .

- E_{RY} lead the E_{RN} by 30 degree

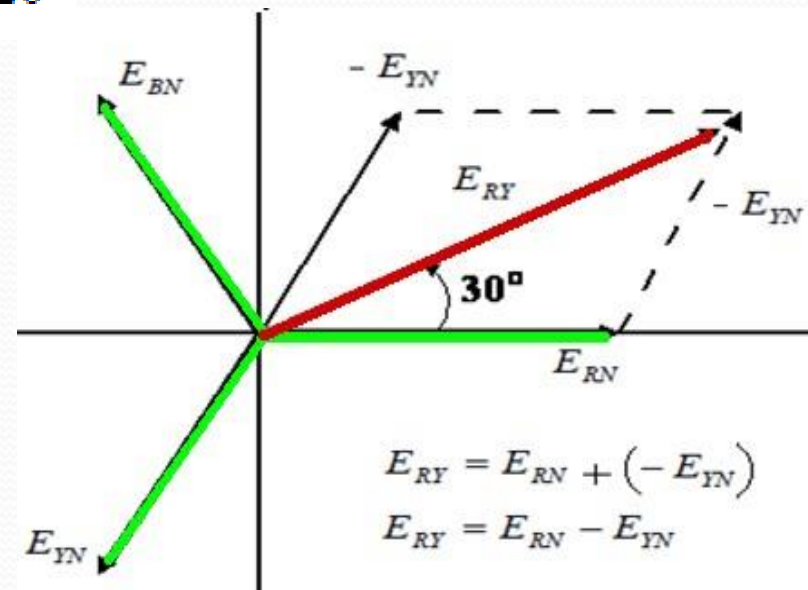

Cont...

- Similarly other line voltages $\mathbf{E_{YB}}$ as shown in brief

$$E_{YB} = E_{YN} - E_{BN} = E \angle -120^\circ - E \angle +120^\circ$$

$$E_{YB} = \sqrt{3}E \angle -90^\circ$$

- The magnitude of the line voltage, is E_{YB} is $\sqrt{3}$ times the magnitude of the phase voltage E_{YN} .
 - E_{RY} lead the E_{RN} by 90 degree
 - Similarly other line voltages $\mathbf{E_{YB}}$ as shown in brief
- $$E_{BR} = E_{BN} - E_{RN} = E \angle +120^\circ - E \angle 0^\circ$$
- $$E_{BR} = \sqrt{3}E \angle +150^\circ$$
- So, the three line voltages are balanced, with their magnitudes being equal, and the phase angle being displaced from each other in sequence by 30.

Relation between the Phase and Line Current for Star Connection

- In the star connected system each line connector is connected to separate phase, so current flowing through the lines and phase
 - Lines Current I_L (I_{RY} , I_{RB} , I_{YB}) = Phase Current I_P (I_{BN} , I_{YN} , I_{RN})
- If the phase current has a phase difference of ϕ with the phase voltage, then
 - Power output per phase = $E_P I_P \cos\phi$
 - Total power output phase = $3 E_P I_P \cos\phi$

$$\therefore E_P = \frac{E_L}{\sqrt{3}}$$



$$= \frac{3 E_L}{\sqrt{3}} I_L \cos\phi$$

$$= \sqrt{3} E_L I_L \cos\phi$$

Currents for Circuits with Balanced Load (Delta-connected)



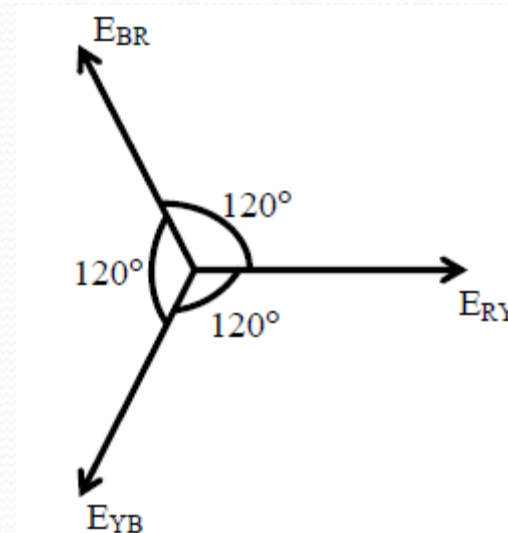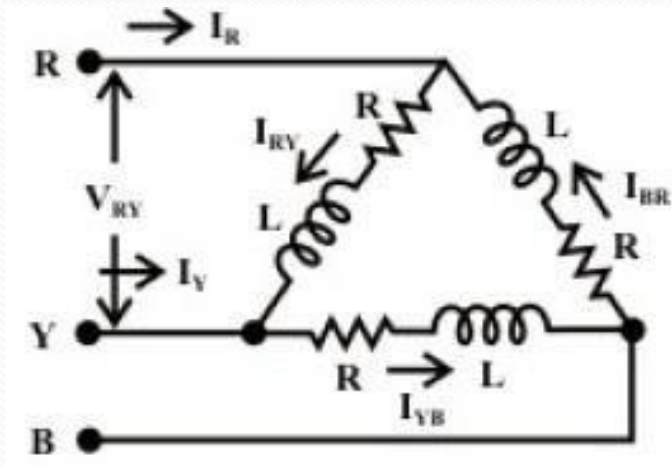
$$E_{RY} = E \angle 0^\circ; \quad E_{YB} = E \angle -120^\circ; \quad E_{BR} = E \angle +120^\circ$$



Delta(Δ)-Star(Y) conversion and Star-Delta conversion

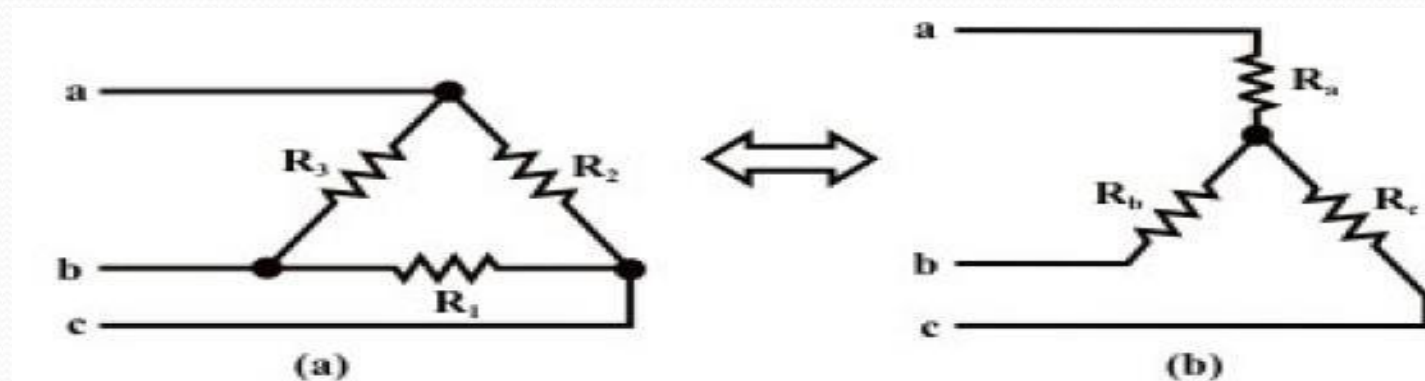- The formulas for delta-star conversion, using resistance



$$R_a = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_3 R_1}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

- The formulas for star-delta conversion, using resistance, are


$$R_1 = R_b + R_c + \frac{R_b R_c}{R_a} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_a}$$

$$R_2 = R_c + R_a + \frac{R_c R_a}{R_b} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_b}$$

$$R_3 = R_a + R_b + \frac{R_a R_b}{R_c} = \frac{R_a R_b + R_b R_c + R_c R_a}{R_c}$$

For impedance conduction

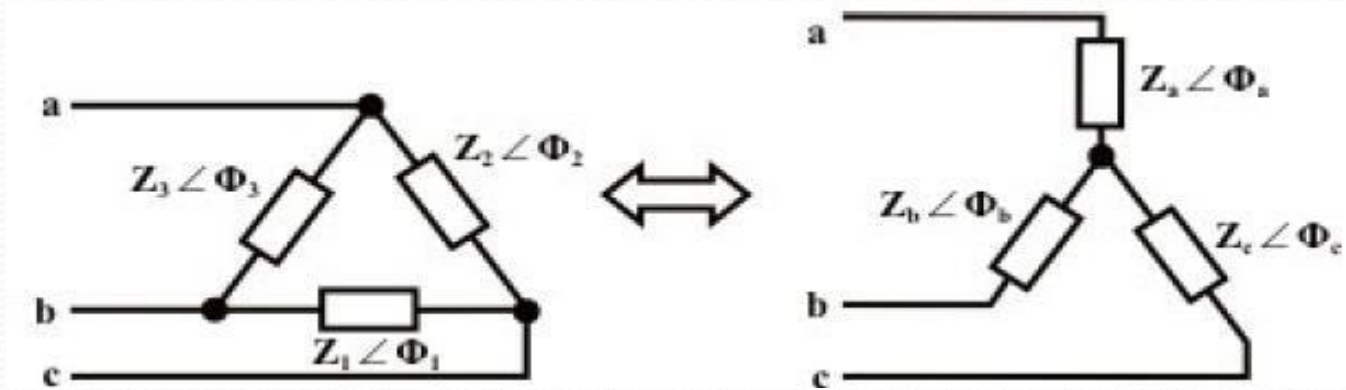- The formulas for delta-star conversion, using impedances.



$$Z_a = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3} \quad Z_b = \frac{Z_3 Z_1}{Z_1 + Z_2 + Z_3} \quad Z_c = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

- The formulas for delta-star conversion, using impedance, are

$$Z_1 = Z_b + Z_c + \frac{Z_b Z_c}{Z_a} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_a}$$

$$Z_2 = Z_c + Z_a + \frac{Z_c Z_a}{Z_b} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_b}$$

$$Z_3 = Z_a + Z_b + \frac{Z_a Z_b}{Z_c} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c}$$



Thank You